



UNIVERSITI
TEKNOLOGI
MALAYSIA
www.utm.my

SCSR1013 DIGITAL LOGIC

MODULE 9: SHIFT REGISTERS

SCHOOL OF COMPUTING



MODULE 9

SHIFT REGISTERS

Objectives:

1. To introduce the characteristics and function of a shift register
2. To highlight different types of shift register
3. To introduce shift register IC
4. To explain shift register counter

MODULE CONTENT

- Basic Shift Register functions
- Shift Register:
 - Serial In/Serial Out (SISO)
 - Serial In/Parallel Out (SIPO)
 - Parallel In/Serial Out (PISO)
 - Parallel In/Parallel Out (PIPO)
- Shift Register counters
 - Ring Counter
 - Johnson Counter

Basic Shift Register (SRG) Functions

- **SRG** is a register in which binary data can be **stored**, and this data can be **shifted** to the left or right when a signal is applied.
- It consist of arrangements of **FFs**.

Module:
Page 34


Memory
Devices in
Digital
Systems

- Digital System : Important in application involving:
 - a) Data storage
 - b) Data transfer / movement


Module:
Page 7

 a) The flip-flop as a storage element

- Each FF can store 1 bit data.
- More bits require more FF.



 
When a 1 is on D , Q becomes a 1 at the triggering edge of CLK or remains a 1 if already.



When a 0 is on D , Q becomes a 0 at the triggering edge of CLK or remains a 0 if already.

 
b) Basic Data Transfer / Movements in SRG.

(Four bits are used for illustration. The bits move in the direction of the arrows.)




(a) Serial in/shift right/serial out

SISO

 


(b) Serial in/shift left/serial out

SISO

 


(c) Parallel in/serial out

PISO

 


(d) Serial in/parallel out

SIPO

 


(e) Parallel in/parallel out

PIPO

 


(f) Rotate right

 

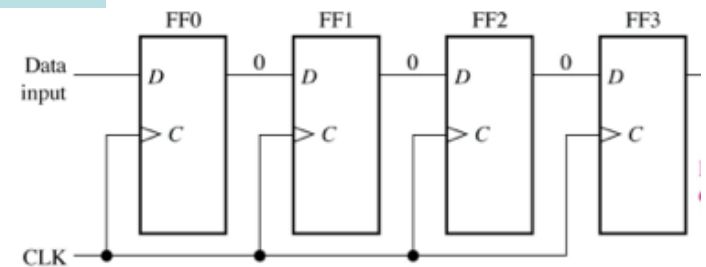(g) Rotate left

- A register can shift data one bit at a time.
- The **logical configuration** of a serial SRG:
 - A chain of FF connected in **cascade**.
- The operation of SRG: **Synchronous**.
 - Using common clock.



Problem : Shifting N bit SRG will lose all data after $2N$ clock cycles.

Solution : Using rotate.

(a) SISO

- Accepts data serially, one bit (input) at a time on a single line
- Each clock pulse will enter one bit data (**Data in**) into SRG and at the same time one bit will be shifted to Q_7
- Output produced in serial form too.



Figure : Logic symbol for an 8-bit serial in/serial out shift register

Example 1:

LSB shifted in first.

1010

- Four bits (1010) being entered serially into the register
- Every clock cycle a data is shifted to the right one position
- For n bit SISO it requires n clock cycle to completely entering the shift register
 - i.e. for the first data entered to appear at the output

 


Figure : Four bits (1010) being serially **shifted out** of the register and replaced by all zeros.


Output:

1 0 1 0


- Once all data is shifted in, every clock cycle will make the data shifted another one position to the right
- On the 5th clock cycle, the first 0 is shifted out and lost, its position replaced by the 2nd data, at the left most flip-flop new data entering the SISO
- This kind of shifting repeats every clock cycle.
- Assuming every time a new data is 0, at the 8th clock cycle all flip-flop in SISO will be replaced by a new data

For n -bit SISO, it requires:

- n clock cycle to **shifted in** all data
- another n clock cycle to **shifted out** all data.

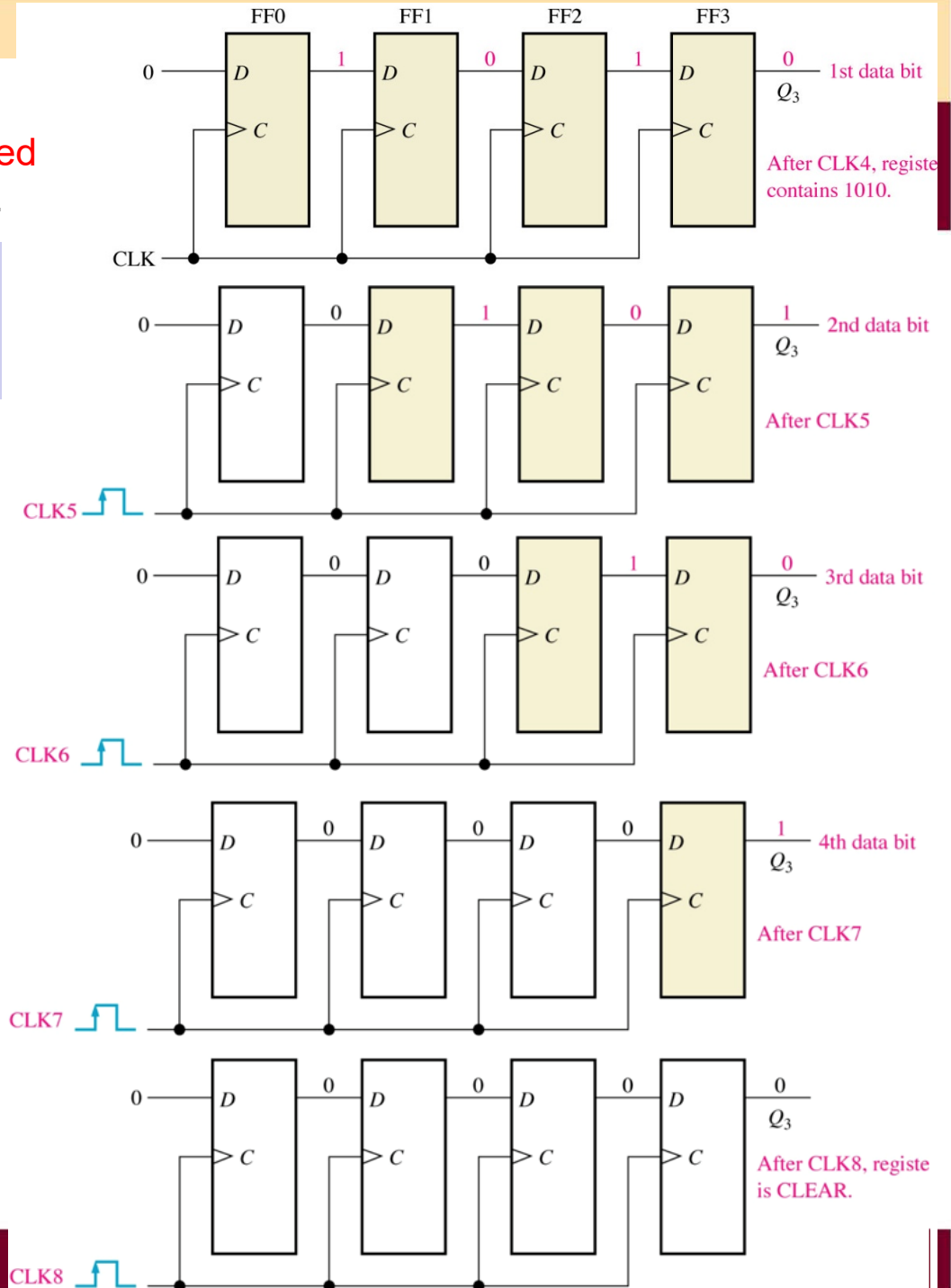

Example 2: SISO

 

MSB
1101
LSB

Data shifted in:

Clock, t	FF0	FF1	FF2	FF3
Initially	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	0	1	1	0
4	1	0	1	1

Bit **MSB** will insert **first**.
The last FF will hold MSB

Data shifted out:

Clock, t	FF0	FF1	FF2	FF3	Data lost
Initially	1	0	1	1	X
5	0	1	0	1	1
6	0	0	1	0	1
7	0	0	0	1	0
8	0	0	0	0	1

Bit MSB will go out first



Example 3:

5-bit SISO (Right SRG)

Data input: **11010**

Initially all FFs are cleared.


MSB are shifted in **first**.

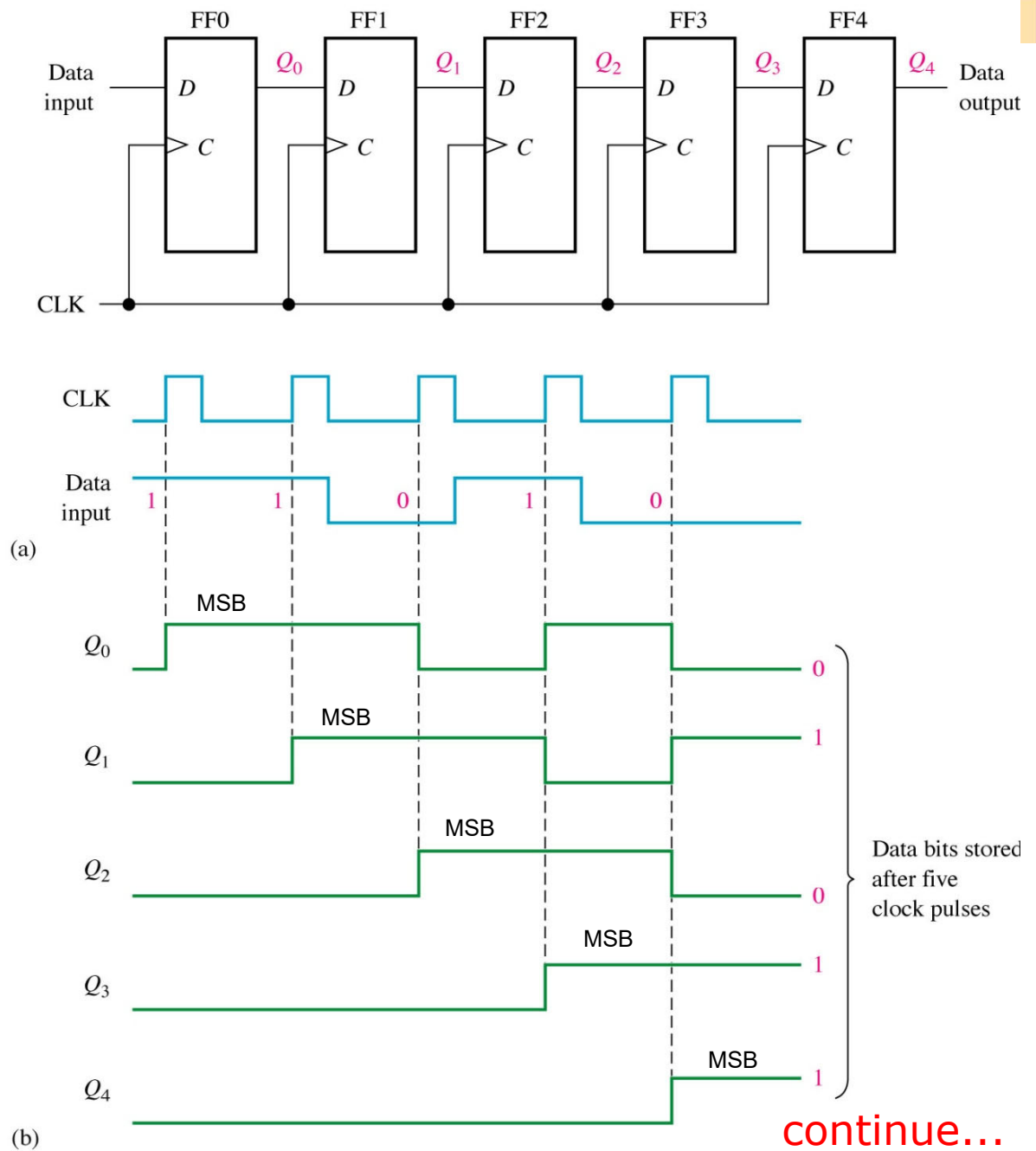 

Data input: **11010**

Self-Test:

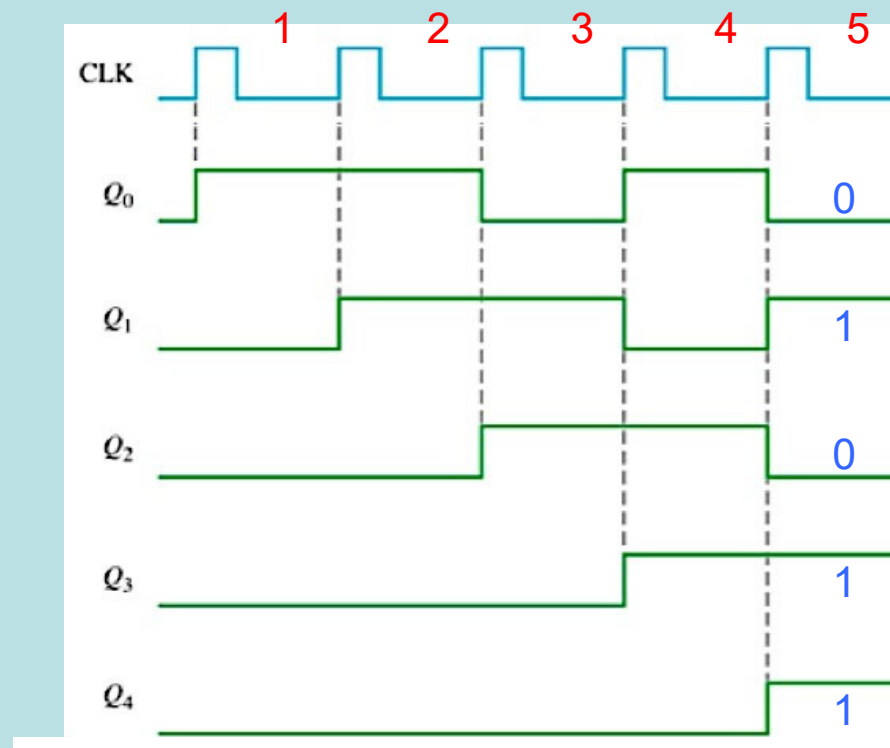
Generate a table for
the data **shifting out**.
(**MSB** shifted out **first**)



Clock, t	FF0	FF1	FF2	FF3	FF4
Initially	0	1	0	1	1
6	0	0	1	0	1
7	0	0	0	1	0
8	0	0	0	0	1
9	0	0	0	0	0
10	0	0	0	0	0

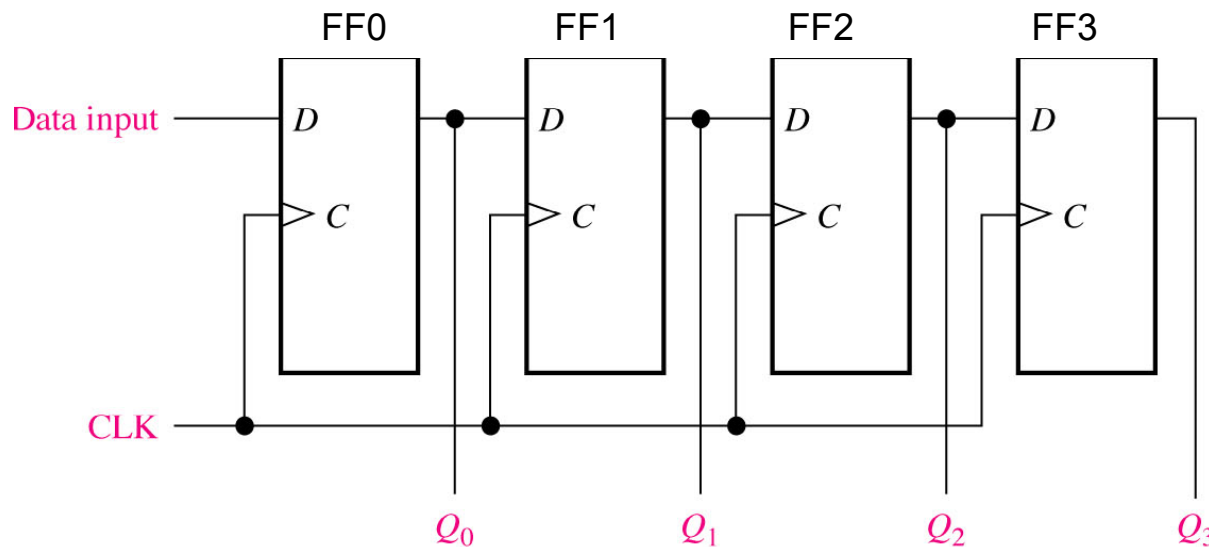
(b) SIPO

- Data bits are **entered serially** one bit at a time.
- **Output** is in **parallel**
 - All bits are available **simultaneously** after n clock cycles for n -bit SIPO.




(a)

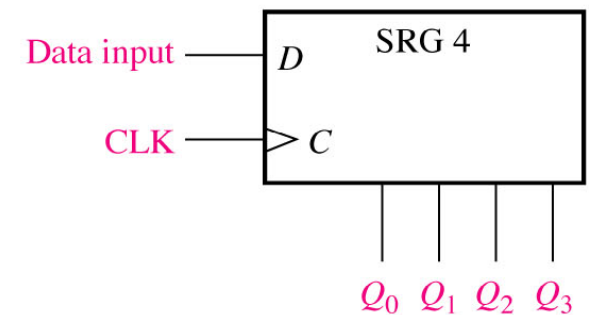For SISO, output only at Q_3 .
For SIPO output $Q_3Q_2Q_1Q_0$




(b)

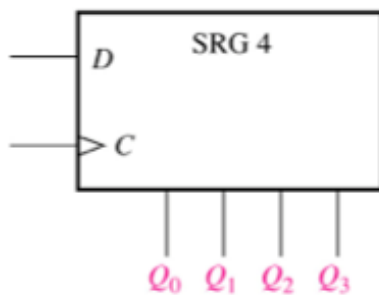Example 4: Show the states of 4-bit SIPO shift register (SRG 4) for the data input **0110** and clock waveforms. The register initially all is 1s.



Clock, t	FF0	FF1	FF2	FF3
Initially	1	1	1	1
1	0	1	1	1
2	1	0	1	1
3	1	1	0	1
4	0	1	1	0

Q_0 Q_1 Q_2 Q_3

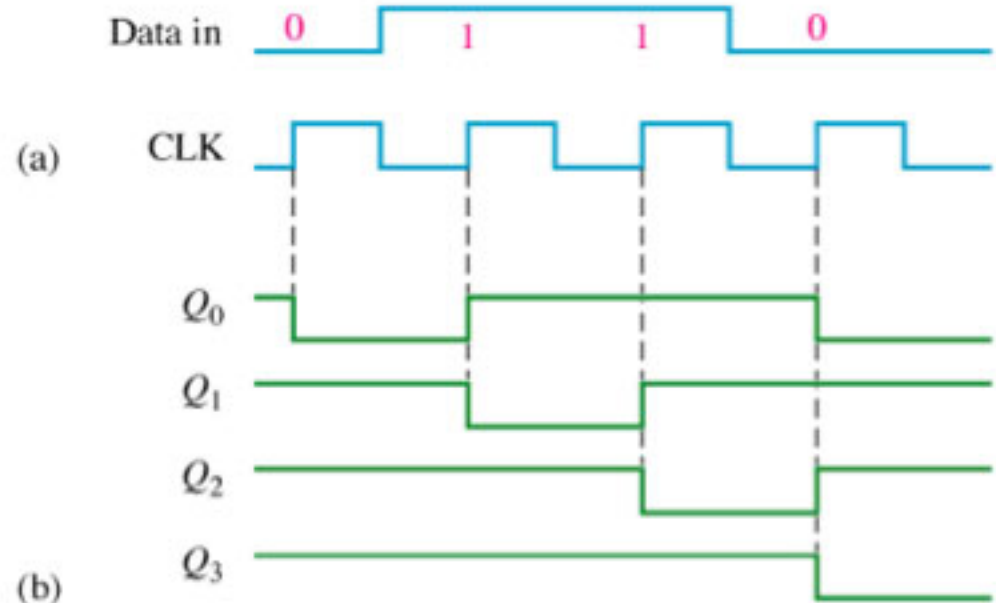

Exercise 9.1: Show the states of 6-bit SIPO shift register (SRG 6) for the data input **011001** and clock waveforms.
The register initially all is 0s and MSB will enter first.

Exercise 9.1: Show the states of 6-bit SIPO shift register (SRG 6) for the data input **011001** and clock waveforms.

The register initially all is 0s and **MSB** will enter **first**.

Solution :

Clock, t	FF0	FF1	FF2	FF3	FF4	FF5
Initially	0	0	0	0	0	0
1	0	0	0	0	0	0
2	1	0	0	0	0	0
3	1	1	0	0	0	0
4	0	1	1	0	0	0
5	0	0	1	1	0	0
6	1	0	0	1	1	0



Q_0



Q_1



Q_2



Q_3



Q_4




Q_5


... data input **011001**

Clock, t	FF0	FF1	FF2	FF3	FF4	FF5
Initially	0	0	0	0	0	0
1	0	0	0	0	0	0
2	1	0	0	0	0	0
3	1	1	0	0	0	0
4	0	1	1	0	0	0
5	0	0	1	1	0	0
6	1	0	0	1	1	0


Clock waveform

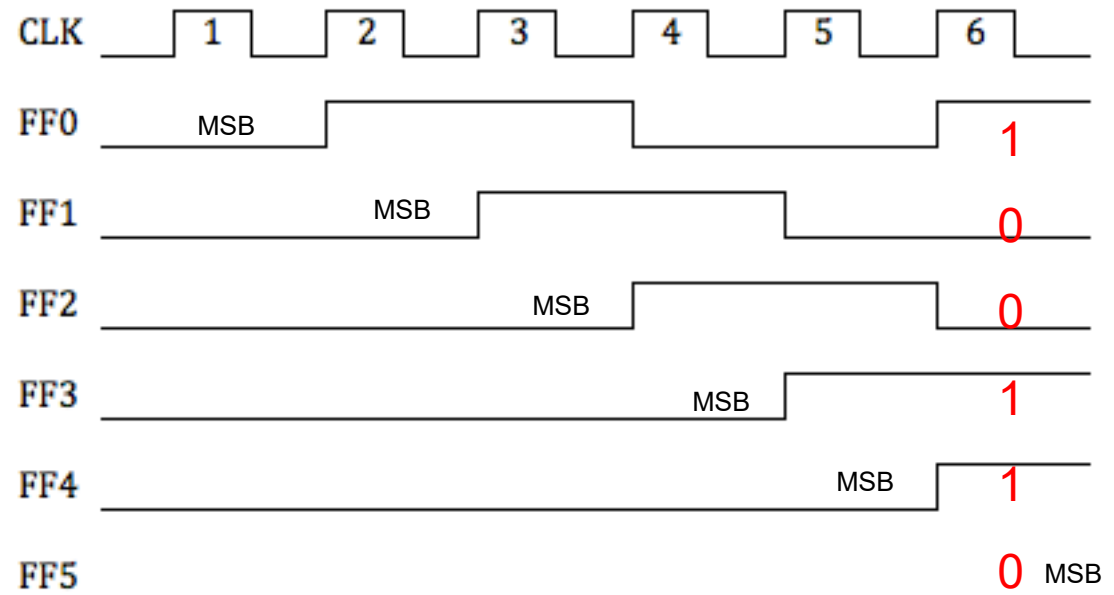

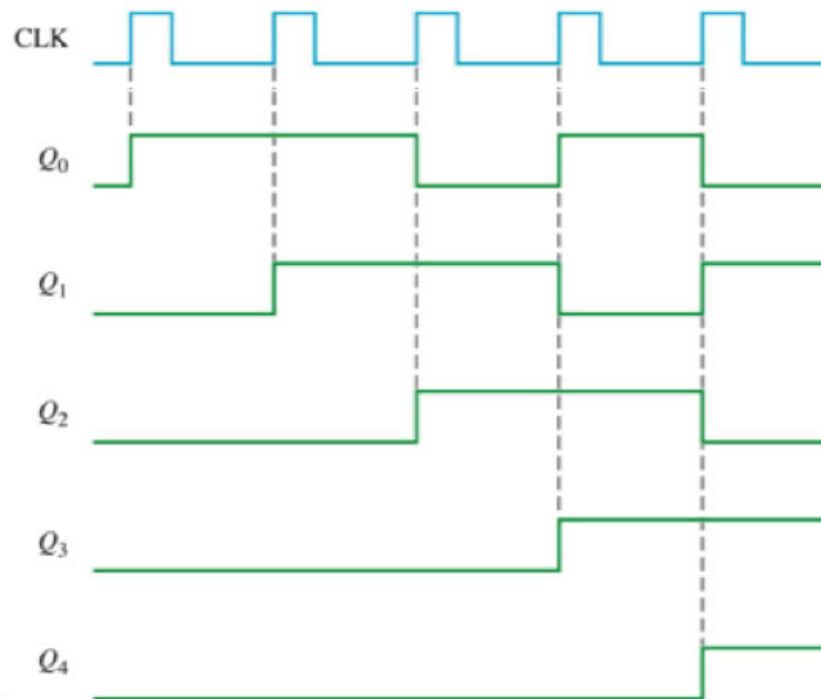- Exercise 9.2:**
- a) Determine how many bit entered to the SIPO register?
 - b) Circle on the timing diagram the valid output.
 - c) Determine the data entered. (Assume MSB shifted in first)



 - Exercise 9.2:**
- a) Determine how many bit entered to the SIPO register?
 - b) Circle on the timing diagram the valid output.
 - c) Determine the data entered. (Assume **MSB** shifted in **first**)




Solution:

a) 5 bits

b) The valid output

c) 11010

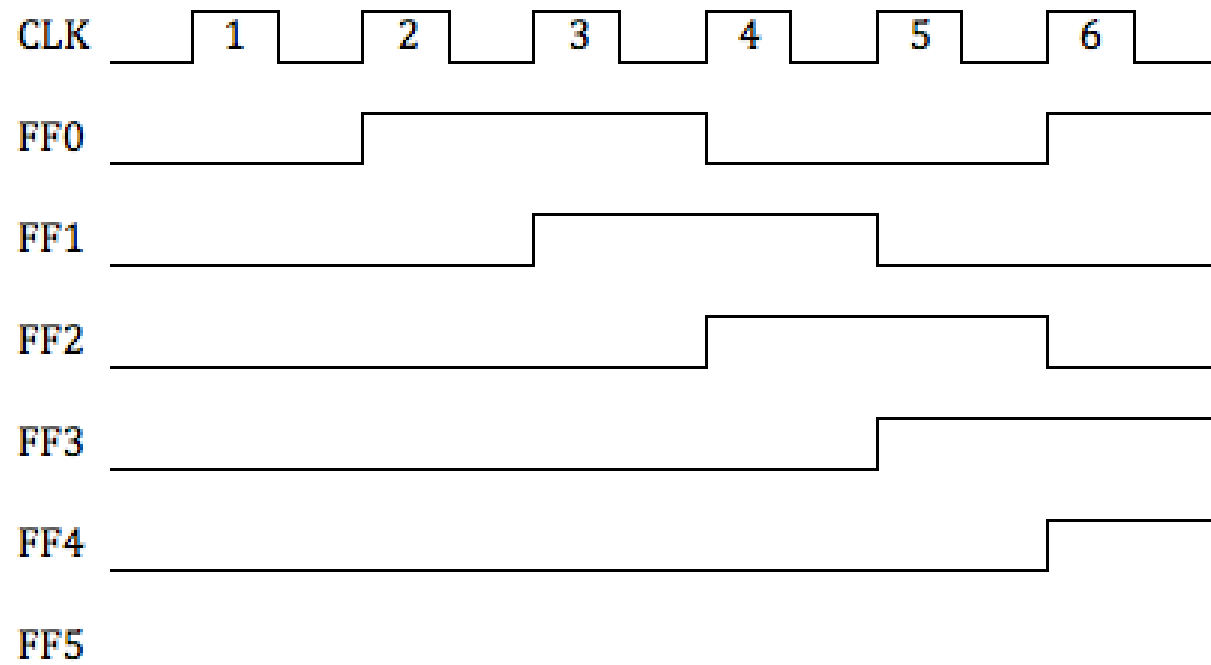- Exercise 9.3:**
- a) Determine how many bit entered to the SIPO register?
 - b) Circle on the timing diagram the valid output.
 - c) Determine the data entered. (Assume **LSB** shifted in first)




- Exercise 9.3:**
- a) Determine how many bit entered to the SIPO register?
 - b) Circle on the timing diagram the valid output.
 - c) Determine the data entered. (Assume **LSB** shifted in first)

Solution:

a) 6 bits


b) The valid output:

c) 100110

 

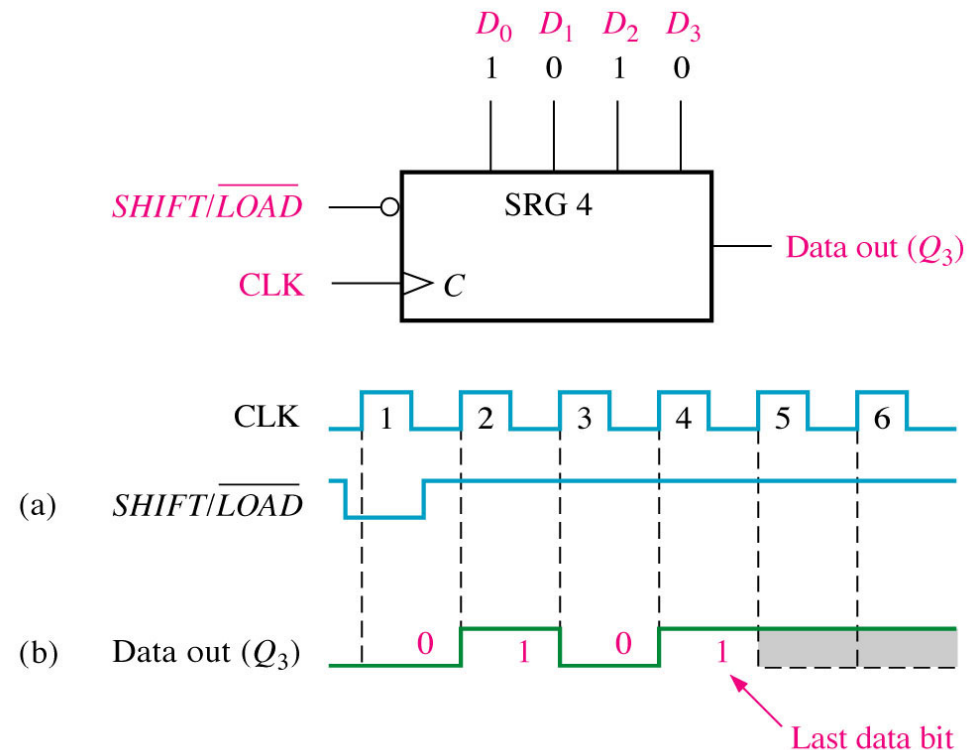(c) PISO

- Inputs entered **simultaneously** (**in parallel**) into respective stages on parallel lines
- Outputs are one bit at a time (**serial**)
- Modes: *SHIFT / \overline{LOAD}*




Mode	Value	Function
LOAD	0	Loads the input values
SHIFT	1	Shifts them out at clock pulse

NOTES:


- Input pins: $D_3D_2D_1D_0$
- MSB appear at Data out (Q_{n-1})
- After $n+1$ clock cycle, all n bits data will lost.

Exercise 9.4: Complete the timing diagram of 6-bit PISO shift register (SRG 6) for the data input **011001**. The register initially all is 0s and assume **MSB** shifted out **first**.

 a) Draw the shift register logic symbol with the inputs.




b) Complete the timing diagram.

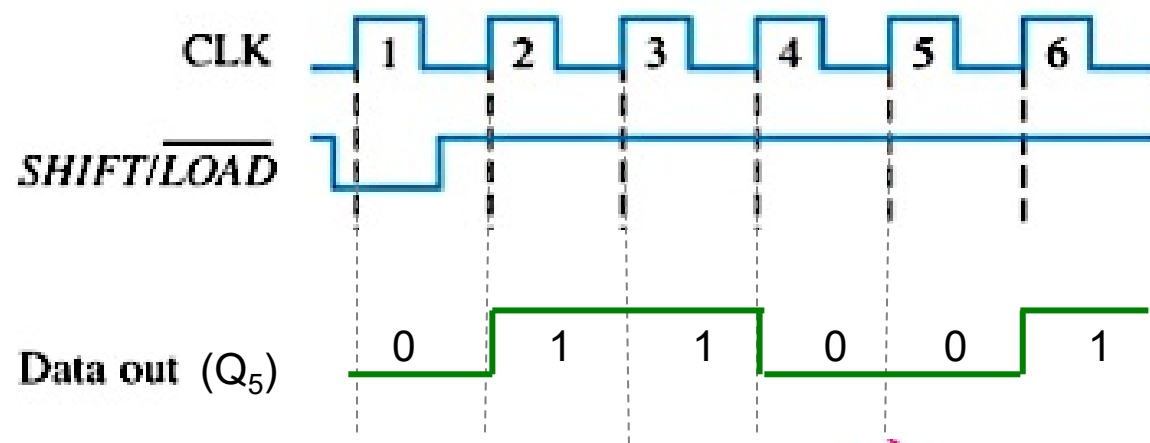

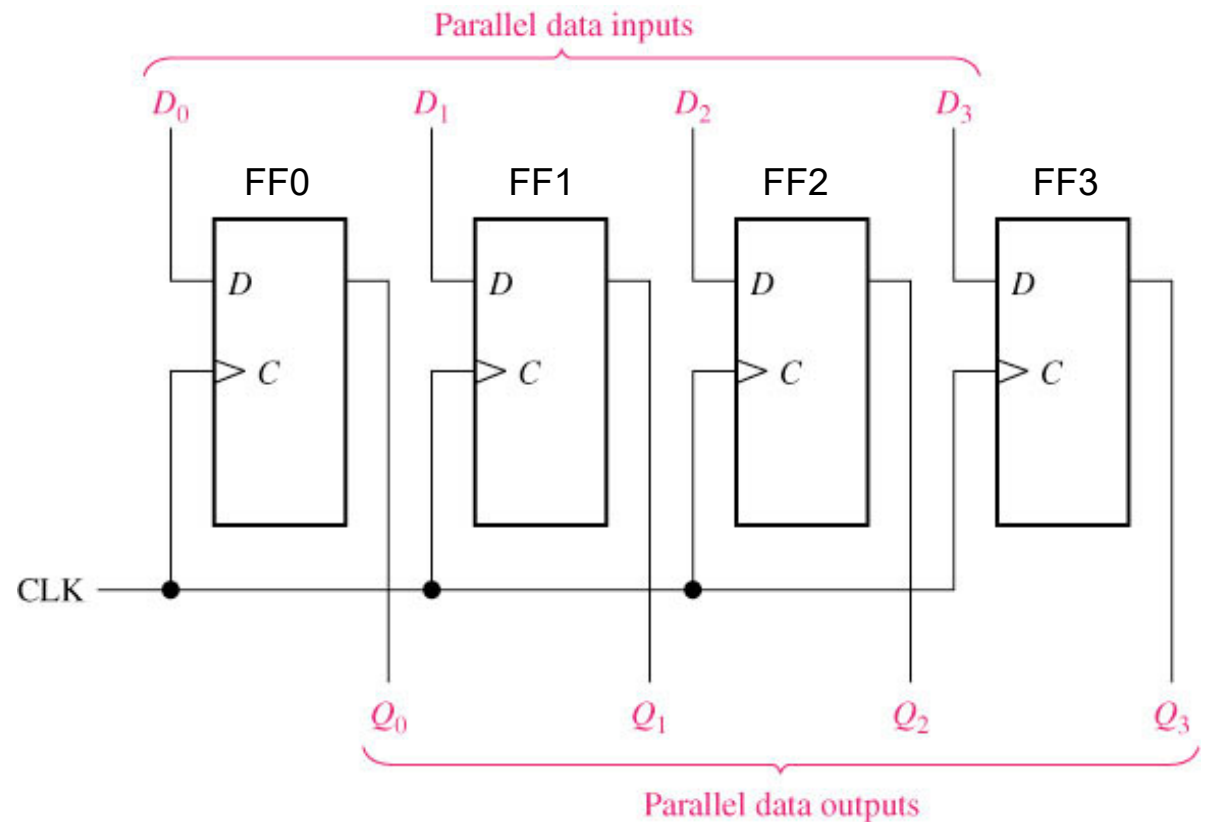(d) PIPO

- Input and output done in parallel.
- Enter all inputs - Bits appear on the parallel outputs





UTM
UNIVERSITI TEKNOLOGI MALAYSIA


www.utm.my

Shift Register Counters

Shift Register Counter


- A shift register with serial output connected back to the serial input to produce special sequences.
- In normal counter, to provide individual digit outputs instead of a binary or BCD output.
 - adding a **decoder**.
- But much simpler to use a different counter structure with simple decoder
 - **Shift Registers (SR)**

- 2 most common types:

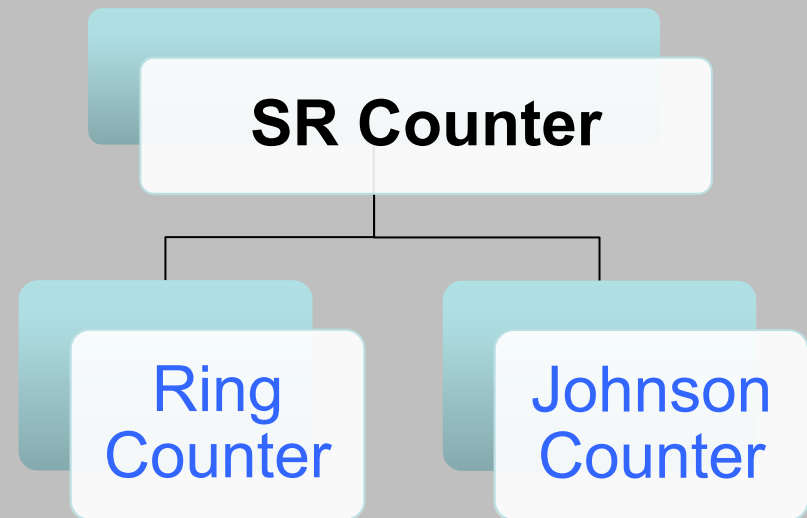


Shift Register Counter: (a) Ring Counter

 - A type of **SISO shift register** but final output is **fed back** to the first input.



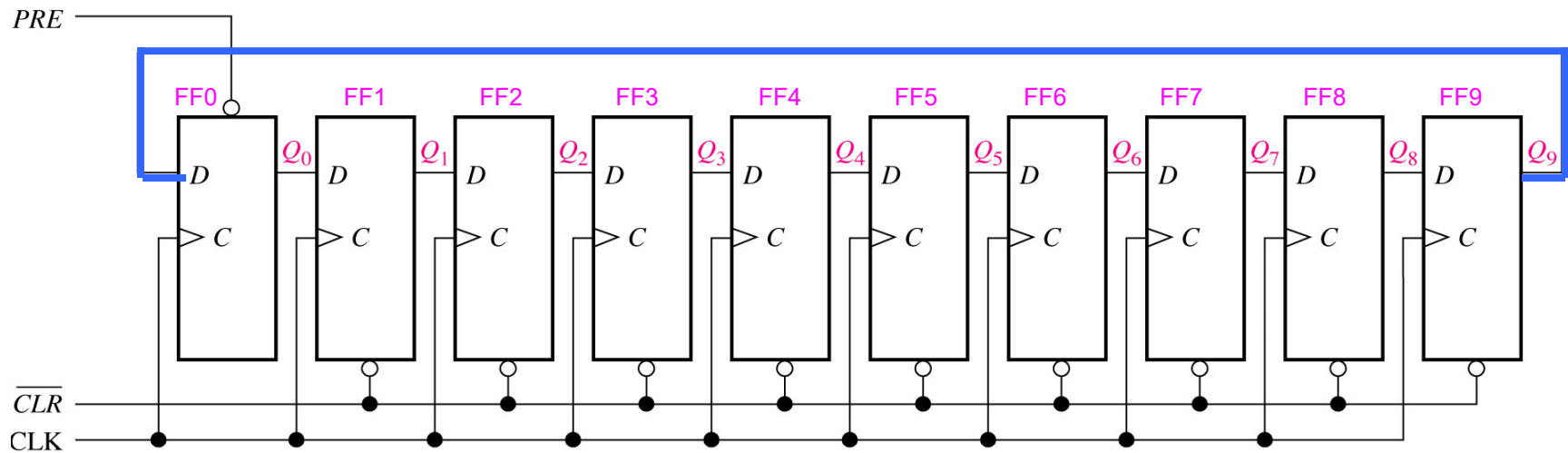(a) Serial in/shift right/serial out

- The ring counter uses 1 FF for each state in its sequence
- For a **10-bit ring counter**, there is a unique output for each decimal digit



$n\text{-bit} = \text{MOD } n$
(state number)

Example:


- For a 10-bit ring counter, there are 10 FFs which make a **MOD 10 counter**.
- It will **recycle** after 10 clock cycles.

Example 7: If a 10-bit ring counter has the initial state 0000000101, determine the waveform for each of the Q outputs.

Solution:

D_9	D_8	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	1	0	1


MSB LSB

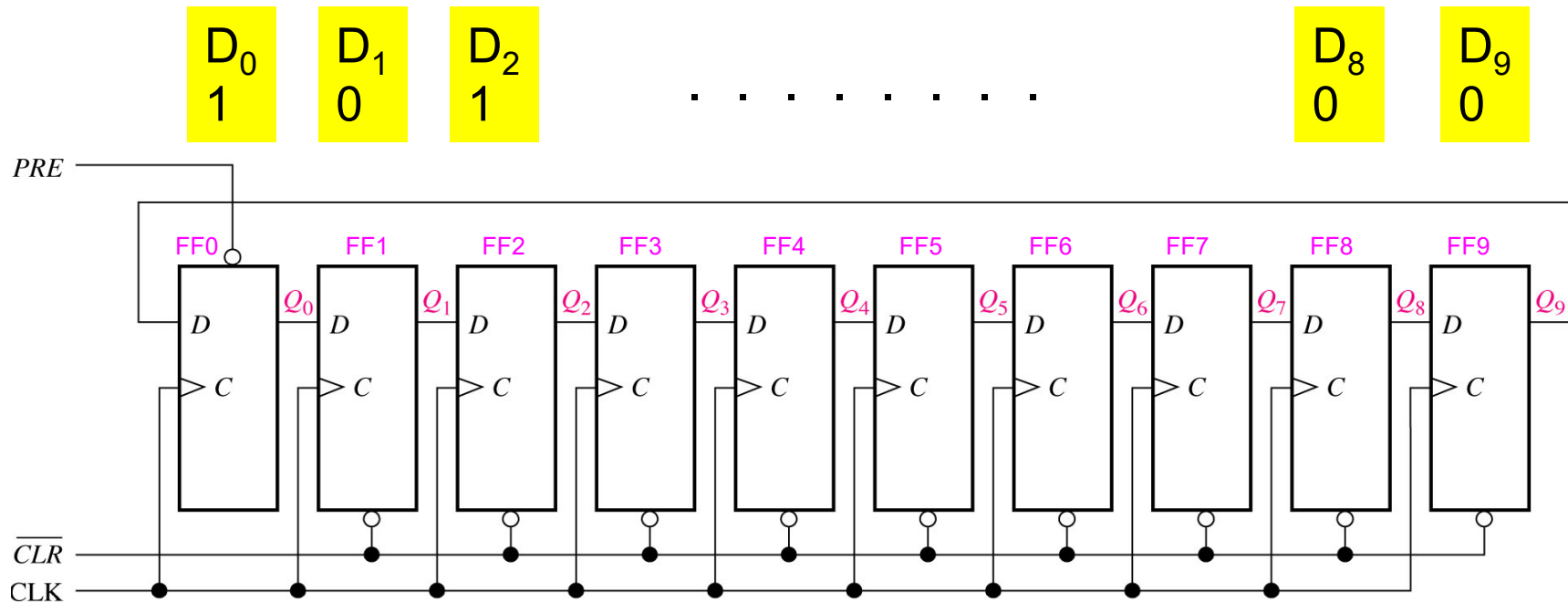

D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	1	0	1

MSB

LSB

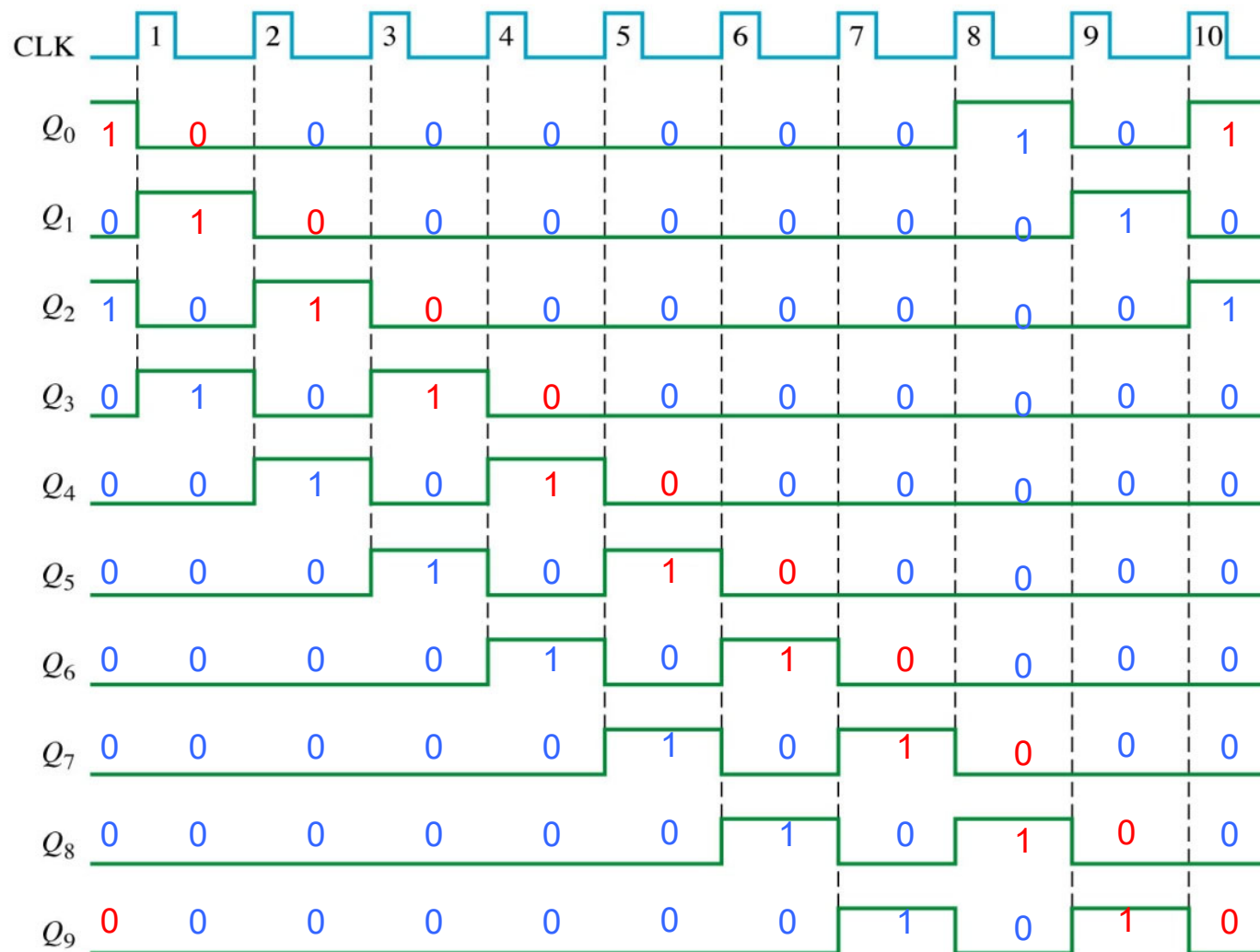

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2										
3										
4										
5										
6										
7										
8										
9										

Q₉

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3										
4										
5										
6										
7										
8										
9										

Q₉

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4										
5										
6										
7										
8										
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5										
6										
7										
8										
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6										
7										
8										
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6	0	0	0	1	0	1	0	0	0	0
7										
8										
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6	0	0	0	1	0	1	0	0	0	0
7	0	0	0	0	1	0	1	0	0	0
8										
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6	0	0	0	1	0	1	0	0	0	0
7	0	0	0	0	1	0	1	0	0	0
8	0	0	0	0	0	1	0	1	0	0
9										

Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6	0	0	0	1	0	1	0	0	0	0
7	0	0	0	0	1	0	1	0	0	0
8	0	0	0	0	0	1	0	1	0	0
9	0	0	0	0	0	0	1	0	1	0



Clock Pulse	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Q ₇	Q ₈	Q ₉
0	0	0	0	0	0	0	0	1	0	1
1	1	0	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	0	1
3	1	0	1	0	0	0	0	0	0	0
4	0	1	0	1	0	0	0	0	0	0
5	0	0	1	0	1	0	0	0	0	0
6	0	0	0	1	0	1	0	0	0	0
7	0	0	0	0	1	0	1	0	0	0
8	0	0	0	0	0	1	0	1	0	0
9	0	0	0	0	0	0	1	0	1	0

Shift Register Counter: (b) Johnson Counter


- In the Johnson counter the last output is complemented and fed back in as an input to the first FF
- Examples shown with **D** FF, but can be implemented with other types of FF as well.
- Number of unique states are **2 times** the number of bits (FF)
 - 4 bits $\rightarrow 4*2 = 8$ states
 - 5 bits $\rightarrow 5*2 = 10$ states
- Johnson counter will produce a modulus of $2n$;
(n = number of stages)
- **modulus 10 a.k.a. mod 10

$$n\text{-bit} = \text{MOD } 2n \\ (\text{state number})$$

$n\text{-bit} = \text{MOD } 2n$
(state number)

 Example (a):


- For a **4-bit** ring counter, there are 4 FFs which make a **MOD 8 counter**.
- It will recycle after 8 clock cycles.



(a) Four-bit Johnson counter

 
Example (b):

- For a **5-bit** ring counter, there are 5 FFs which make a **MOD 10 counter**.
- It will recycle after 10 clock cycles.



(b) Five-bit Johnson counter

Example:

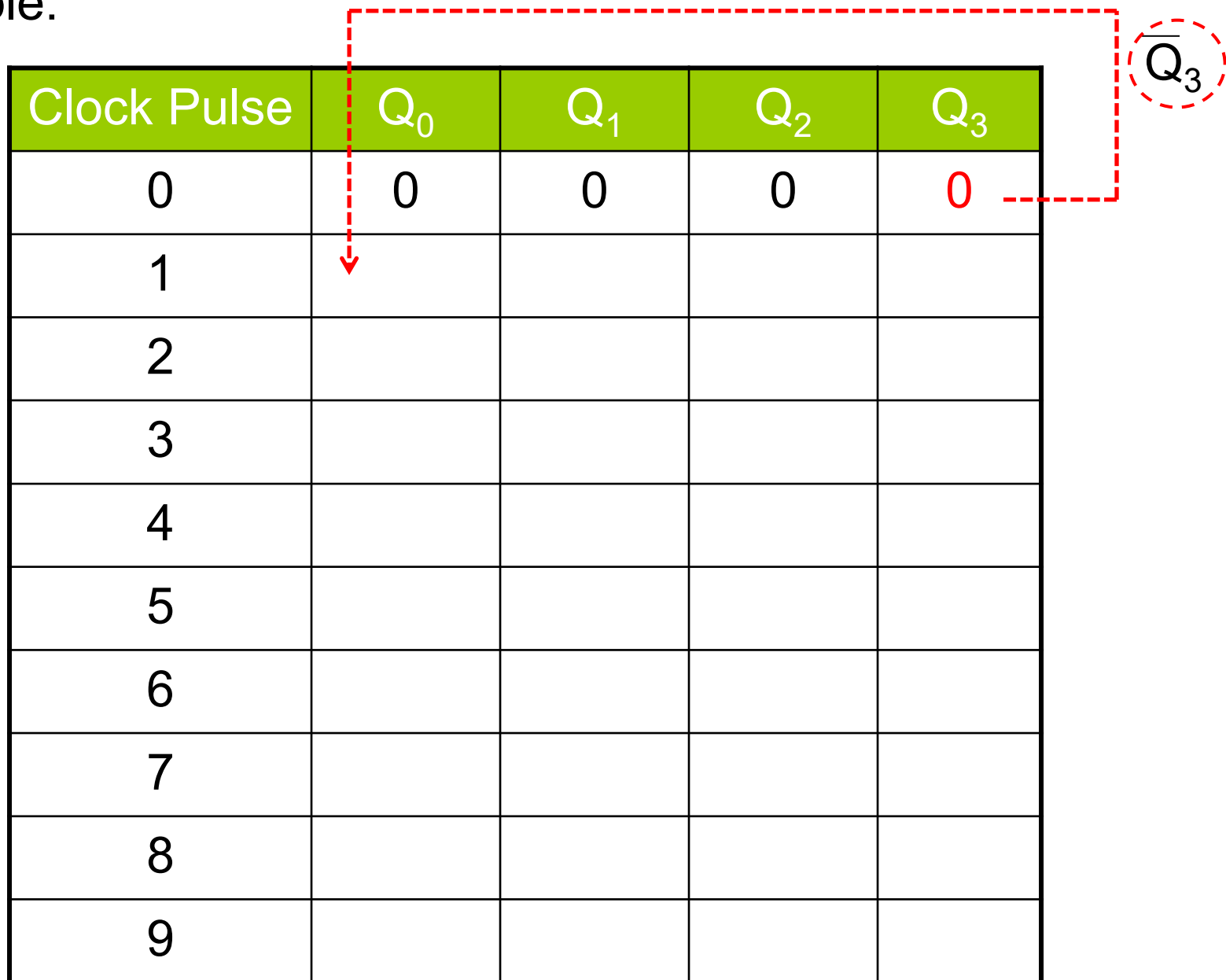

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1				
2				
3				
4				
5				
6				
7				
8				
9				

Example:

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5				
6				
7				
8				
9				

Example:

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8				
9				

Complete
one cycle

Repete
cycle


Example:

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0
9

Complete
one cycle

Repeat
cycle


Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

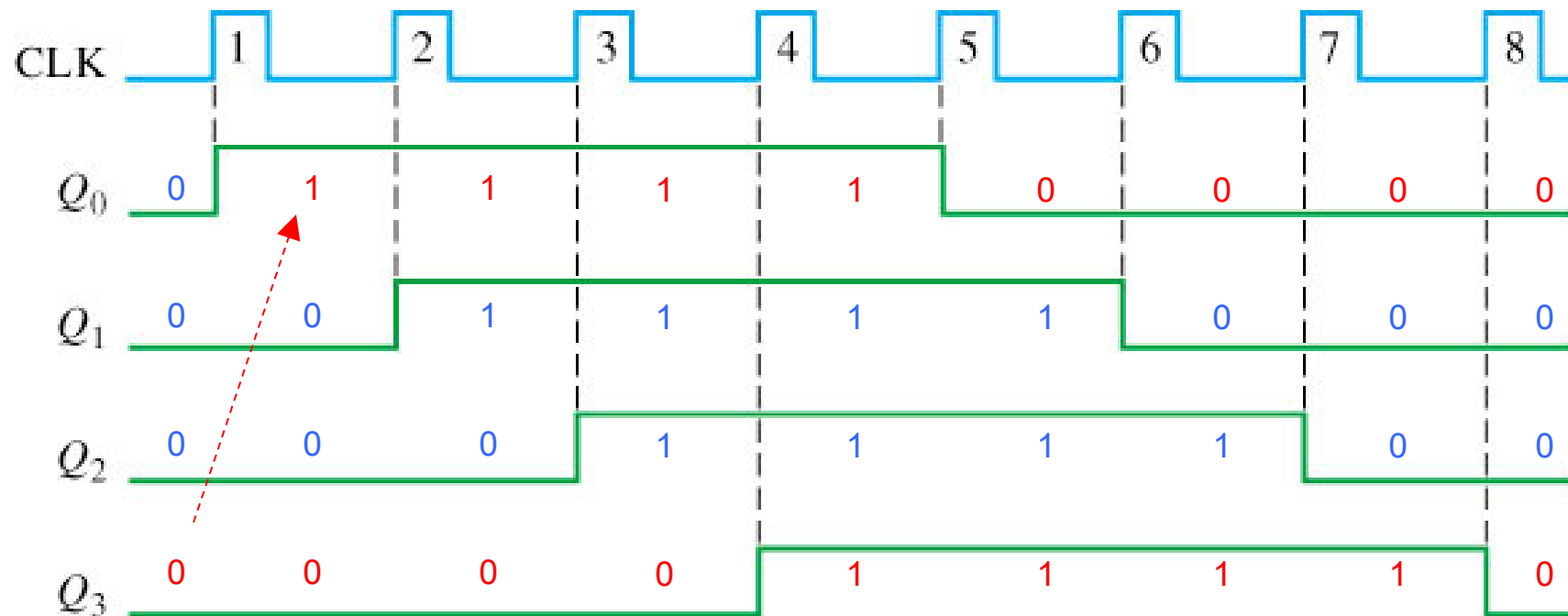


Summary:

Ring Counter

n -bit = MOD n
(state number)

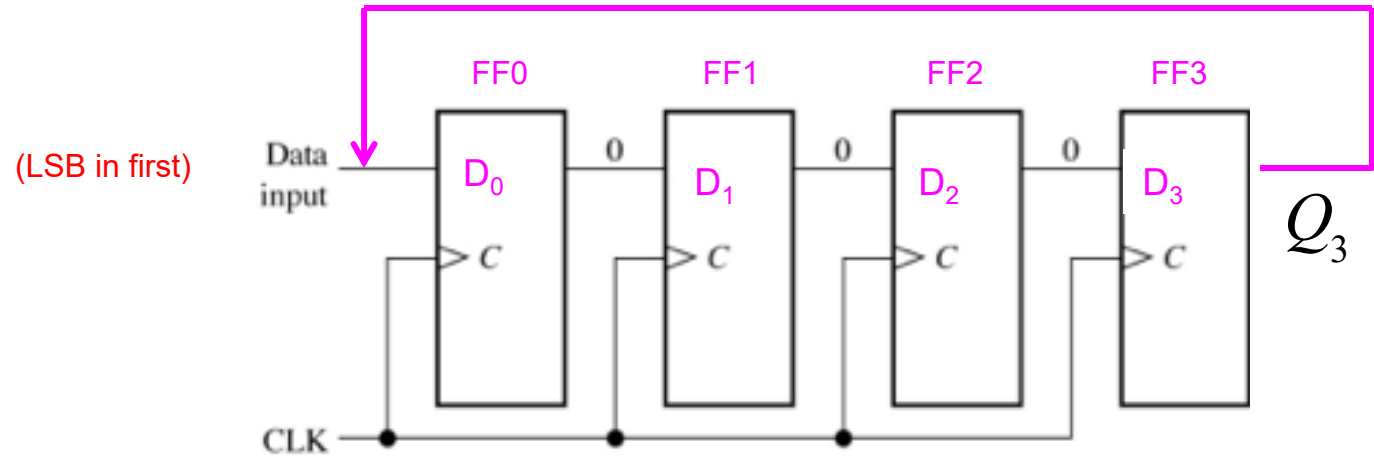


Data representation:

 

Truth Table:

Clock	FF0	FF1	FF2	FF3
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1


State Diagram:

 

Summary: Johnson Counter

(LSB in first)

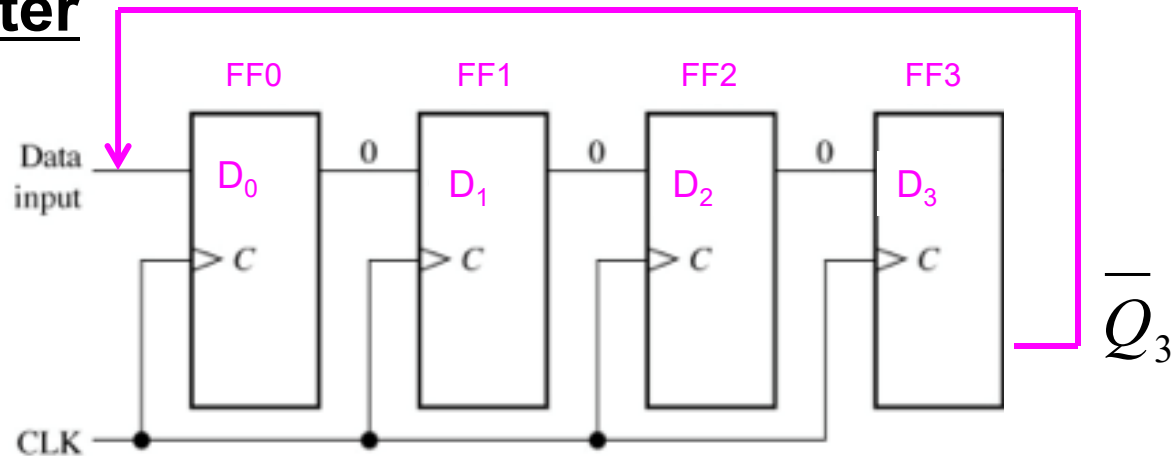
$n\text{-bit} = \text{MOD } 2n$
(state number)




Truth Table:

Clock	FF0	FF1	FF2	FF3
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

Data representation:

 

State Diagram:

 

Summary: Johnson Counter

Clock	FF0	FF1	FF2	FF3
	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

Similar

(Compare to other state)

Other characteristic of Johnson counter:

- Always exist 2 unique bits compared to other state.

Summary: Johnson Counter

Clock	FF0	FF1	FF2	FF3
	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

(Compare to other state)

Similar

Other characteristic of Johnson counter:

- Always exist 2 unique bits compared to other state.

Summary: Johnson Counter

Clock	FF0	FF1	FF2	FF3
	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

(No other states similar; therefore, bit **A** and **B** (i.e. **1** and **0**) are unique)

(Compare to other state)

Other characteristic of Johnson counter:

- Always exist 2 unique bits compared to other state.

Summary: Johnson Counter

Clock	FF0	FF1	FF2	FF3
	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

Other characteristic of Johnson counter:

- Always exist 2 unique bits compared to other state.

Self-Test:

What are the unique bits for the rest of the clocks?

Summary: Johnson Counter

Clock	FF0	FF1	FF2	FF3
	A	B	C	D
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

AND gate is required for output

$$\overline{A}B$$

$$B\overline{C}$$

$$C\overline{D}$$

$$AD$$

$$\overline{A}B$$

$$B\overline{C}$$


$$C\overline{D}$$

$$\overline{A}D$$

Other characteristic of Johnson counter:

- Always exist 2 unique bits compared to other state.
- It will only requires 2 input **AND** decoder to decode a state to an active **HIGH** device.

Example:

 

Comparison of a counter

- For a given n flip-flop, the binary counter can produce the most state and ring is the worst
- In term of decoding , Ring counter is the best because there is no need for a decoder to decode each state, binary counter is the worst because require a more complex decoder
- Johnson always in the middle when comparing those feature

	MOD for n flip-flop	Decoder Input
Ring	n	no need for a decoder
Johnson	$2n$	2 input decoder
Binary	2^n	usually > 2 input decoder

(No. of state)

Self-Test:

1. Given a 3-bit Johnson counter with initial value 000, draw the appropriate sequence table for 7 clock pulses.

Solution:

Clock Pulse	Q_0	Q_1	Q_2
Initial	0	0	0
1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1
6	0	0	0

2. A modulus-10 Ring counter requires a minimum of A.

A) 10 FF

C) 5 FF

B) 20 FF

D) 12 FF

3. A modulus-10 Johnson counter requires B.

A) 10 FF

C) 20 FF

B) 5 FF

D) 12 FF

4. The group of 8 bits $1011\ 0110_2$ is serially shifted (right most bit first, MSB) into an 8-bit parallel output shift register with an initial state of $1110\ 1100_2$. After 2 clock pulses, the register contains C. Assume the first FF is the LSB.

A) $1011\ 0001_2$

C) $1011\ 0010_2$

B) $0100\ 1101_2$

D) $1101\ 1110_2$

5. To serially shift a byte of data into a shift register, there must be B.
- A) 1 clock pulse
 - B) 8 clock pulses
 - C) 8 load pulses
 - D) one clock pulse for each 1 in the data
6. To parallel load a byte of data into a shift register with a synchronous load, there must be A.
- A) 1 clock pulse
 - B) 8 clock pulses
 - C) 8 load pulses
 - D) one clock pulse for each 0 in the data



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

END OF DIGITAL LOGIC

MODULES



FINAL

SCSR1013 Digital Logic

(Module 6, 7, 8, 9)

9 February 2023 (Thursday) || 2:30 pm – 5:30 pm

Dewan Sultan Iskandar (DSI)