



UNIVERSITI  
TEKNOLOGI  
MALAYSIA  
[www.utm.my](http://www.utm.my)

# SECR1013 DIGITAL LOGIC

## MODULE 7: LATCHES & FLIP-FLOPS

FACULTY OF COMPUTING



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

## Objectives:

- To introduce the various types of latches and flip-flop;
- To explain the characteristic of latches and flip-flop;
- To illustrate the timing diagram associated with each latches and flip-flop operations.

# Topics Outline:

## LATCH

- S-R Latch
- Gated S-R Latch
- Gated D Latch

## FLIP-FLOPS

- S-R Flip-Flop
- J-K Flip-Flop
- D Flip-Flop
- T Flip-Flop



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

---


# Introduction to Latch & Flip-Flop

---


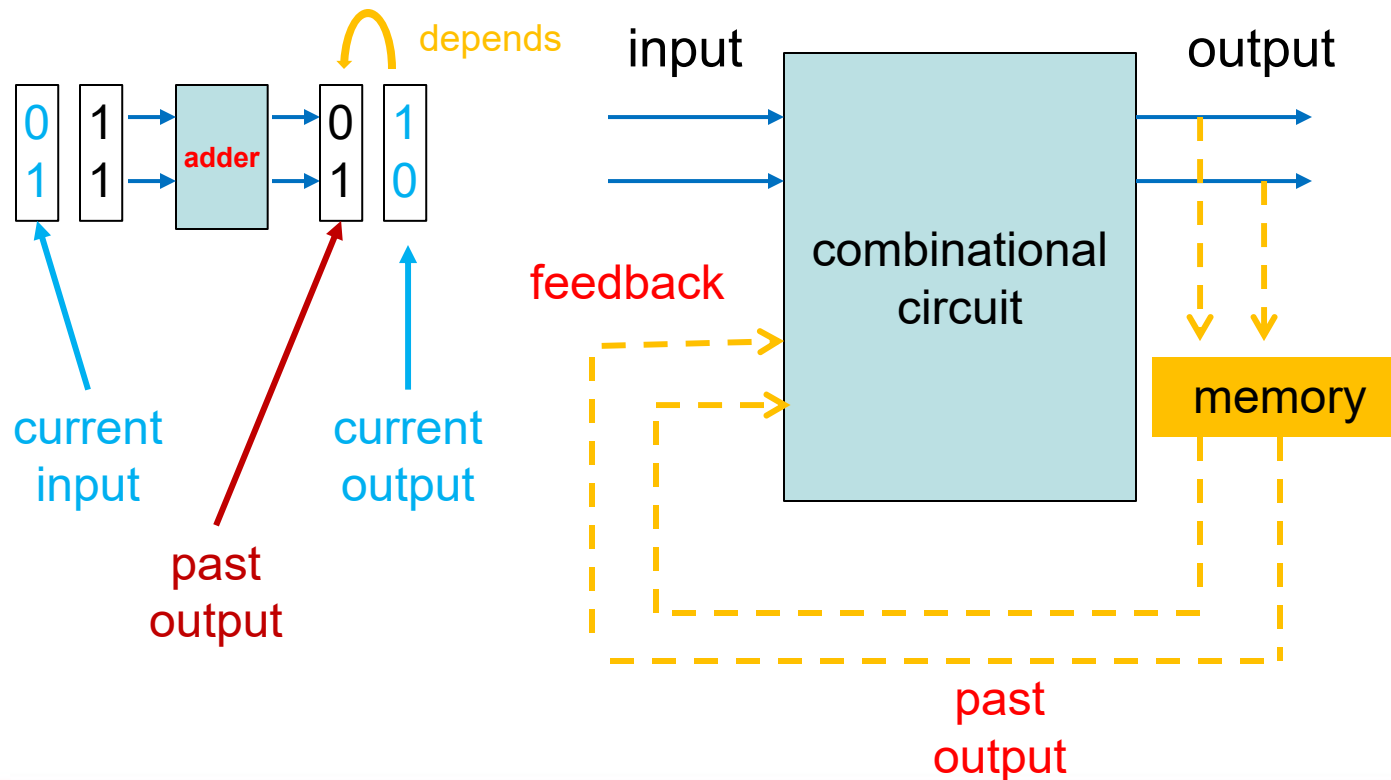
# Introduction

- In **sequential circuits**, the current output depends on the current input as well as past output / outputs



Example of seq. circuits:  
a) flip flop  
b) counter  
c) register

counter  
0 to 5

0: 0  
1: 0 + 1  
2: 1 + 1  
3: 2 + 1  
4: 3 + 1  
5: 4 + 1

# Sequential Vs Combinational Logic Circuit

unlock:

Combinational Logic Circuit:




key sequence is NOT matter

- The output depend on the input
- It has no memory element
  - Therefore, it cannot memorize the previous output



## Sequential Logic Circuit:

 

unlock:

4 → 5 → 6 → 7




To unlock:  
key sequence is MATTER

- It has memory element
- The output depend on the input, as well as the previous output from the feedback elements

Sequential Logic circuits can be divided into 3 main categories:

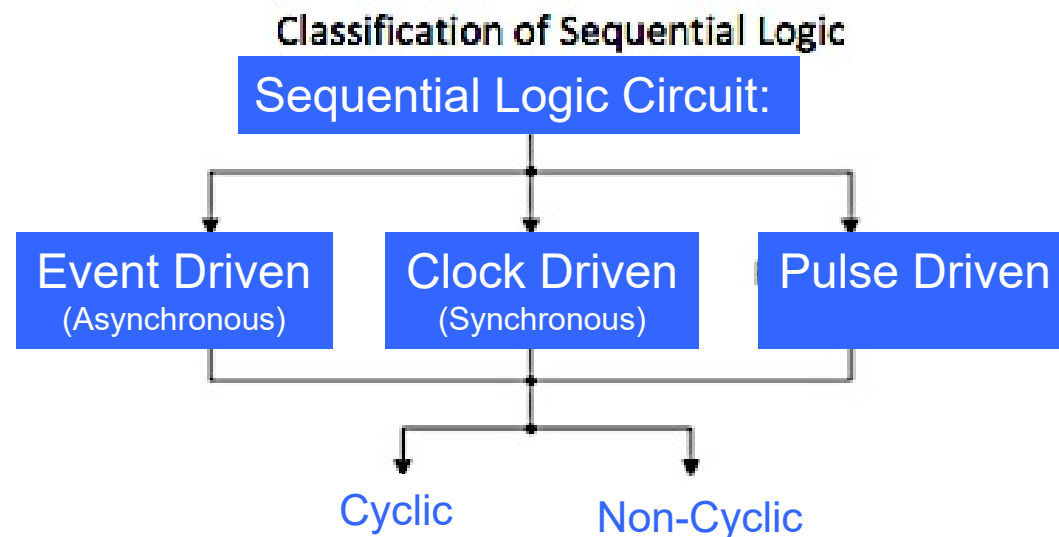1. Clock Driven - Synchronous Circuits that are synchronized to a specific clock signal.
2. Event Driven - Asynchronous Circuits that react or change state when an external event occurs.
3. Pulse Driven - Which is a Combination of Synchronous and Asynchronous.



Sequential logic circuits that return back to their original state once reset, i.e. circuits with loops or feedback paths are said to be "Cyclic" in nature.





**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

---

# Latches

---

# Latch

- **Latch** is a type of temporary storage device
- It has **two stable** states (bi-stable).
- Latch is level sensitive, or level-triggered.
  - are dependent on the voltage level applied (0/1), not on any signal transition.
- Type of Latch :
  - i) **S-R**
  - ii) **Gated S-R**
  - iii) **Gated D**

LOW

HIGH

*INFO :*

A **bi-stable** state is one with *two-stable* output states.


**S** → Set

**R** → Reset


**D** → Data
 
## (i) S-R Latch

- The output of each gate is connected to an input of the opposite data.
- This produces a **regenerative feedback**.




(a) Active-HIGH input S-R latch

 


(b) Active-LOW input  $\bar{S}$ - $\bar{R}$  latch

## S-R Latch: Logic symbol

 


(a) Active-HIGH input  
S-R latch

 

 (b) Active-LOW input  
 $\bar{S}$ - $\bar{R}$  latch


Circuit (a) Active-HIGH input S-R latch :



- use NOR gate
- Input R and S
- Output Q and Q'


Circuit (b) Active-LOW input S'-R' latch :

 - use NAND gate
- Input S' and R'
- Output Q and Q'



### Active-HIGH

INPUTS		OUTPUTS		COMMENTS
$S$	$R$	$Q$	$\bar{Q}$	
0	0	NC	NC	No change. Latch remains in present state
0	1	0	1	Latch RESET
1	0	1	0	Latch SET
1	1	0	0	Invalid condition

 


### Explanation :



- The Q and Q-bar outputs are supposed to be in **opposite** states.
- **Q=1** and Q-bar=0 is defined as **Set** (by making S=1 and R=0)
- **Q=0** and Q-bar=1 is defined as **Reset** (by making S=0 and R=1)
- When S and R are both equal to **0**, the latch's outputs **Not Change** in their prior states.
- If Q and Q-bar happen to be forced to the same state (both 0 or both 1), that state is referred to as **invalid**.

### Active-LOW

INPUTS		OUTPUTS		COMMENTS
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state


 


## Example: S-R Latch (Active HIGH)

  

Logic symbol

continue...

  

Logic symbol


## Explanation:

Location	S	R	Q	State
(a)	1	0	1	SET
(b)	0	0	1	HOLD
(c)	0	1	0	RESET
(d)	0	0	0	HOLD
(e)	0	1	0	RESET
(f)	0	0	0	HOLD
(g)	1	0	1	SET




Extra

 **Exercise 7.1:** If the  $\bar{S}$  and  $\bar{R}$  waveform in (a) are applied to the inputs of latch (active-LOW), determine the waveform that will be observed on the Q output in (b). Assume that Q is initially LOW.




# Active-LOW

INPUTS		OUTPUTS		COMMENTS
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state

 

Logic symbol

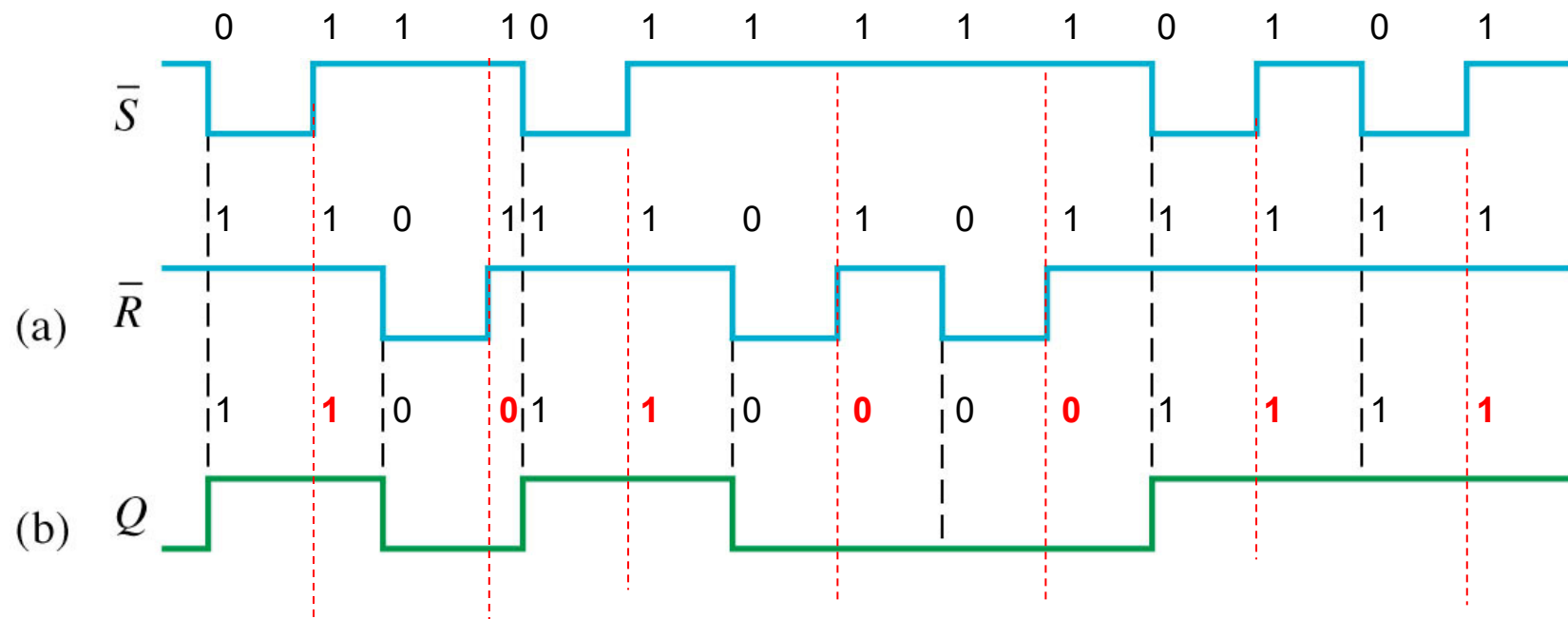
**Solution:** (Red 0/1 is no change or hold)



Extra
 
### Self-Test:

Define when the states are *set*, *reset*, *hold* or *invalid* from the output waveform for each of the inputs.




Extra
 
### Self-Test:

Write the sequence of the states (*set*, *reset*, *hold* or *invalid*) for the output Q waveform for all inputs from the beginning.

Set → Hold → Reset → Hold → Set → Hold → Reset → Hold → Reset → Hold → Set → Hold → Set → Hold



## (ii) Gated S-R Latch


- Is a SR Latch controlled by an **enable input** (EN) switch.
- The S and R inputs control the state to which the latch will function when a **HIGH** level is **applied** to the **EN** input.
- The latch will **not change** until **EN** is **HIGH**, and as long as it remains HIGH, the output is controlled by the state of the S and R input.
- The **invalid state** occurs when **both** S and R are simultaneously **HIGH**.

### INFO :

EN = 1, Latch is On  
EN = 0, Latch is Off


## Gated S-R Latch: Truth Table

EN	S	R	Output, Q
0	0/1	0/1	No Change
1	0	0	No Change
1	0	1	Q=0 (Reset)
1	1	0	Q=1 (Set)
1	1	1	Invalid

 


Logic symbol

 **Example:** Gated S-R Latch.  
Find the waveform for Q.  
Assume that Q is initially LOW.




INPUTS		OUTPUTS	
$S$	$R$	$Q$	$\bar{Q}$
0	0	NC	NC
0	1	0	1
1	0	1	0
1	1	0	0

 **Solution:** Assume that  $Q$  is initially LOW.





Logic symbol

 



## Exercise 7.2:

  

Referring to logic diagram above, fill in the table. Assume initially  $Q = 0$  and  $Q' = 1$



$\overline{S \cdot EN} \quad \overline{R \cdot EN}$					
EN	S	R	Y	Z	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

# Active-LOW

INPUTS		OUTPUTS		COMMENTS
$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

  

**Solution:**

Referring to logic diagram above, fill in the table. Assume initially  $Q = 0$  and  $Q' = 1$


$Q \rightarrow$  Run as 'Active Low S-R' latch when  $EN = 1$

		$\overline{S \cdot EN}$		$\overline{R \cdot EN}$		STATE
EN	S	R	Y	Z	Q	
0	0	0	1	1	0	Hold
0	0	1	1	1	0	Hold
0	1	0	1	1	0	Hold
0	1	1	1	1	0	Hold
1	0	0	1	1	0	Hold
1	0	1	1	0	1	Set
1	1	0	0	1	0	Reset
1	1	1	0	0	-	Invalid



$EN=0$

$EN=1$

 **Example:** Gated S-R Latch.  
Find the waveform for Q.  
Assume that Q is initially LOW.




  **Solution:** Assume that Q is initially LOW.



Self-Test:

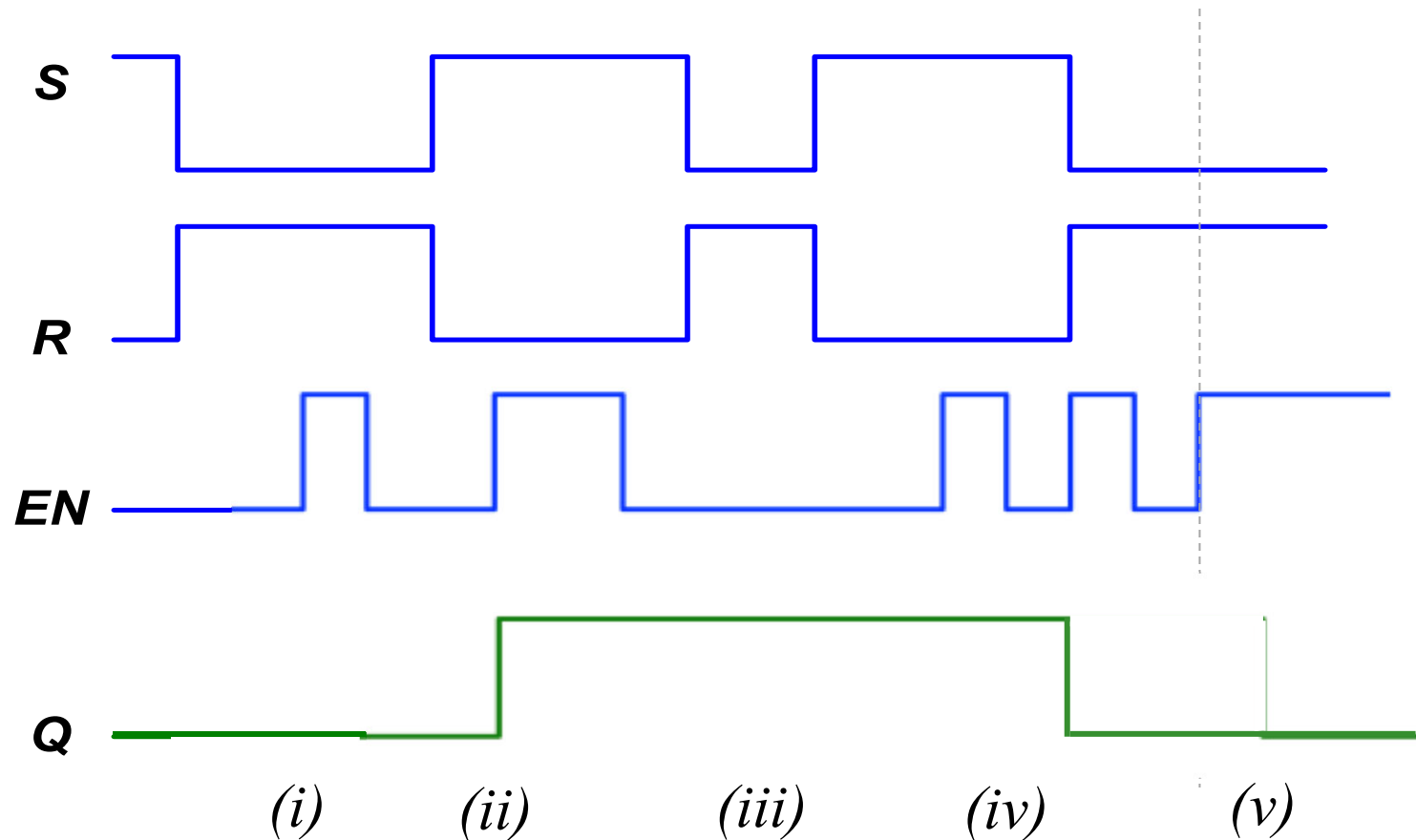Define the states (*set*, *reset*, *hold* or *invalid*) for all outputs waveform  $Q$  that label as  $i$ ,  $ii$ ,  $iii$ ,  $iv$  and  $v$ .



**Solution:**


*(i) Reset*

*(ii) Set*


*(iii) Hold / No change*

*(iv) Hold / No change*


*(v) Reset*

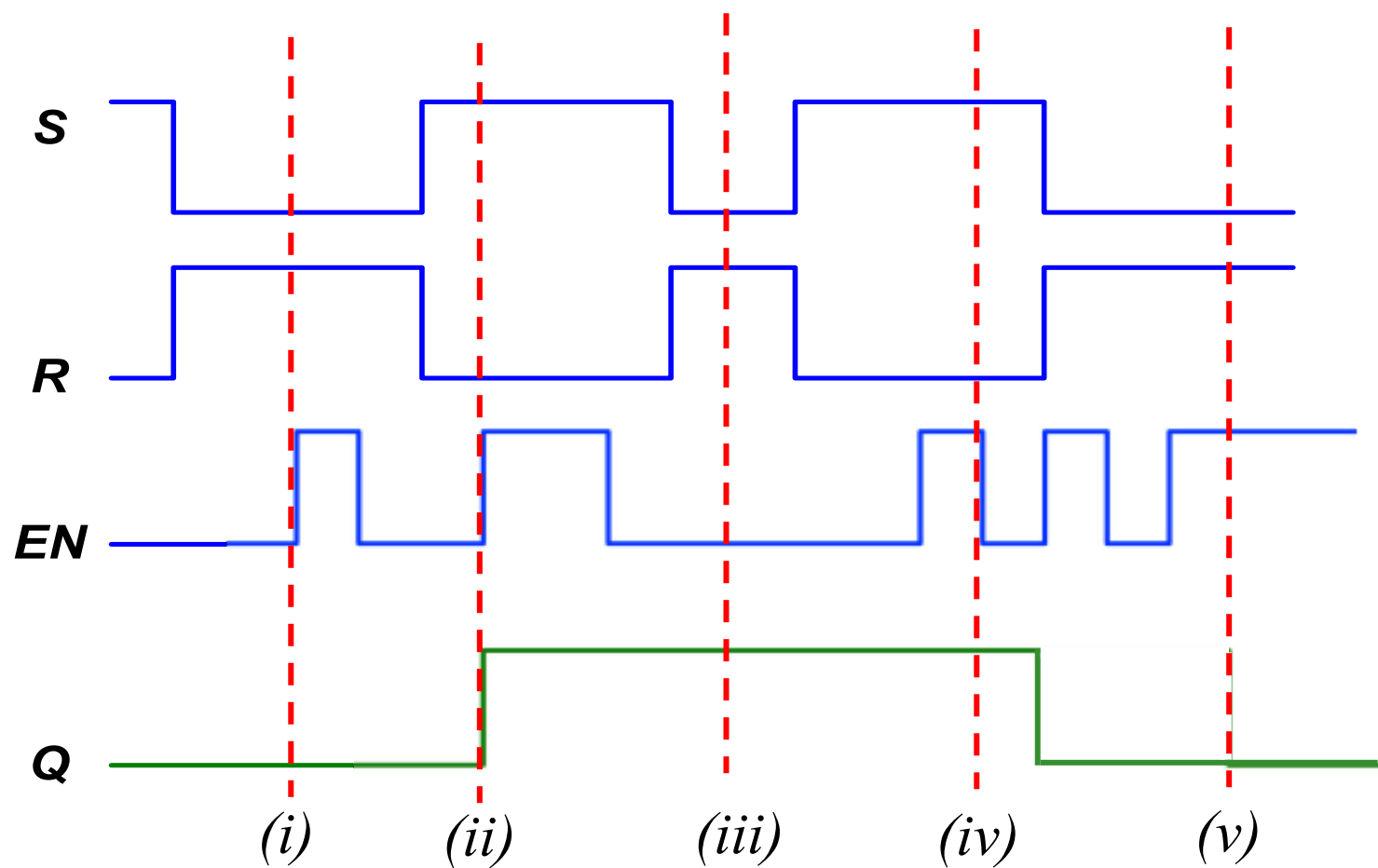
 
### (iii) Gated D Latch: Logic diagram & logic symbol




(a) Logic diagram


 


(b) Logic symbol


## Gated D Latch

 

Modified Gated S-R Latch

  


Gated D Latch

 



## Gated D Latch:

 

The purpose of the inverter is to make sure that  $R$  is the complement of  $S$  and  $R$  will never be the same as  $S$ . So that, we have only two condition at the input of SR.

**Condition 1:**  $D = 0$ , therefore  $S = 0$ ,  $R = 1$  which make  $Q = 0$

**Condition 2:**  $D = 1$ , therefore  $S = 1$ ,  $R = 0$  which make  $Q = 1$

Just like gated SR, when  $EN=0$ , the output does not change. BUT, if  $EN=1$ , the output will depend on the value of input  $D$ .

So, we can conclude that  $Q=D$  when  $EN=1$ .


$$EN=1 \rightarrow Q=D$$

## Gated D Latch: Truth Table


EN	D	Output, Q
0	0	No Change
0	1	No Change
1	0	Q = 0
1	1	Q = 1

EN = 1, Latch is On  
EN = 0, Latch is Off

EN = 1  $\rightarrow$  Q = D

 


 **Example:** Gated D Latch.  
Find the waveform for Q.  
Assume that Q is initially LOW.




Solution:

EN	D	Output
0	0	No Change
0	1	No Change
1	0	$Q = 0$
1	1	$Q = 1$

 

Logic symbol

 



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

---

# Flip-Flops

---




- **Flip-flops (FF)** are **synchronous** bi-stable storage devices capable of storing one bit, where the **output** state only **changes at** a specified point on a **triggering input** called the **Clock (C)**.
- FFs are **edge-triggered**, means that the output changes are synchronized with the **Clock** signal. This may either be
  - a **LOW-to-HIGH** (rising edge) transition or
  - a **HIGH-to-LOW** (falling edge) transition
- Type of Flip-Flops:
  - i) **S-R**      iii) **J-K**
  - ii) **D**        iv) **T**

# Edge-Triggered FF

 
## KEY TERMS :

Rising edge = positive edge  
Falling edge = negative edge


Flip-flop is an important device in a sequential circuit



(a) Positive-going pulse

 

(b) Negative-going pulse

 


Edge-Triggered FF logic symbol

Difference:

## Latch vs Flip-Flop


activated by level-triggered,  
i.e., HIGH or LOW voltages  
from the input signals

### Latch

 

activated by edge-triggered, i.e., voltage  
transitions from HIGH to LOW or LOW to HIGH  
at the clock signals




### Flip-flop

 






# Type of Flip-Flops

(Positive  
edge-  
triggered)

   

(Negative  
edge-  
triggered)

   


(a) S-R


(b) D

(c) J-K


## (i) S-R Flip-Flop

 

 
(a)  $S = 1, R = 0$  flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



 (b)  $S = 0, R = 1$  flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)



 (c)  $S = 0, R = 0$  flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)




S	R	CLK	Output		Comments
			Q	$\overline{Q}$	
0	0	↑	$Q_0$	$\overline{Q}_0$	No Change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	?	?	Invalid


TRUTH TABLE

↑ = clock transition LOW to HIGH

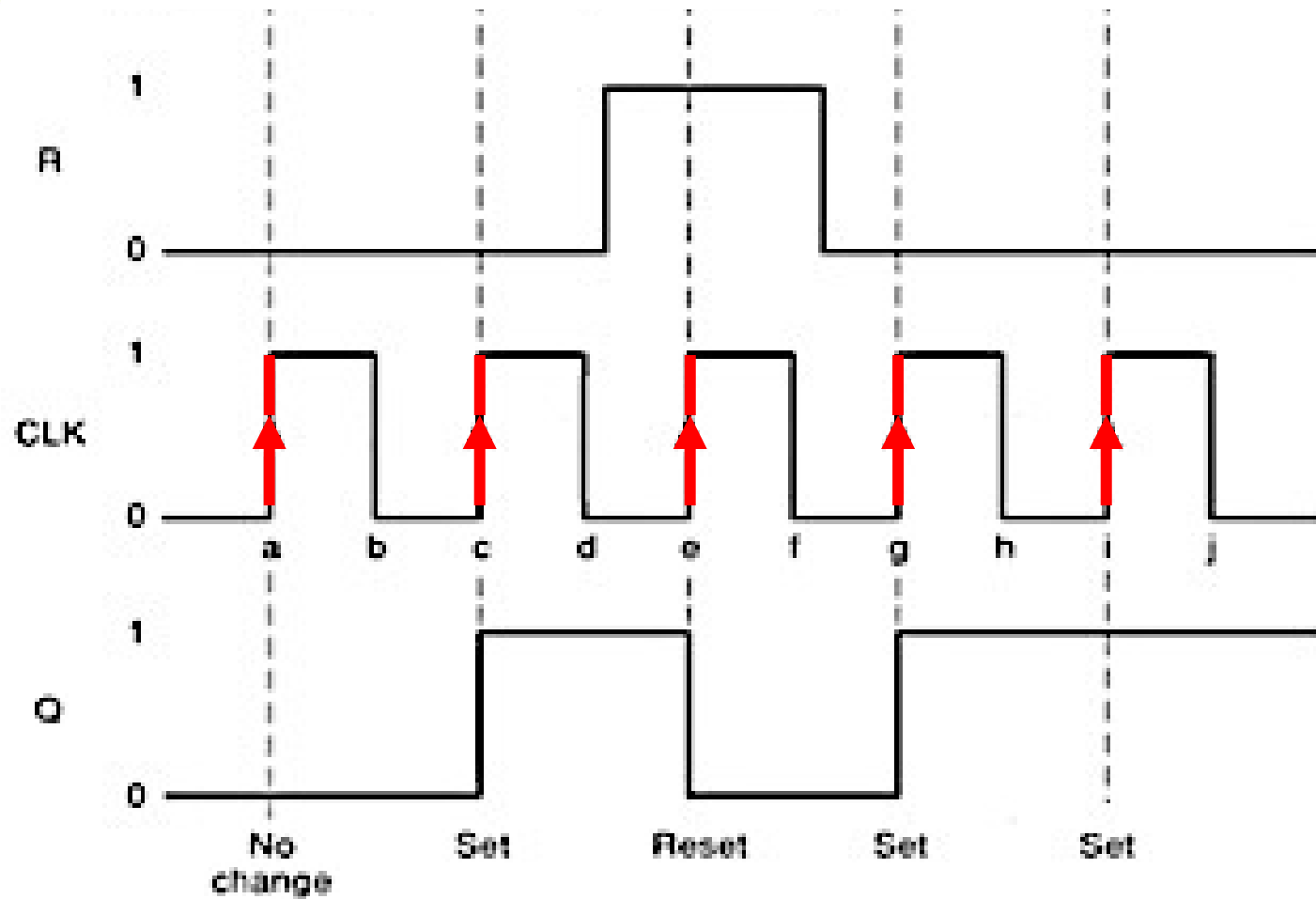$Q_0$  = output level prior to clock transition




*Positive edge-triggered*

 

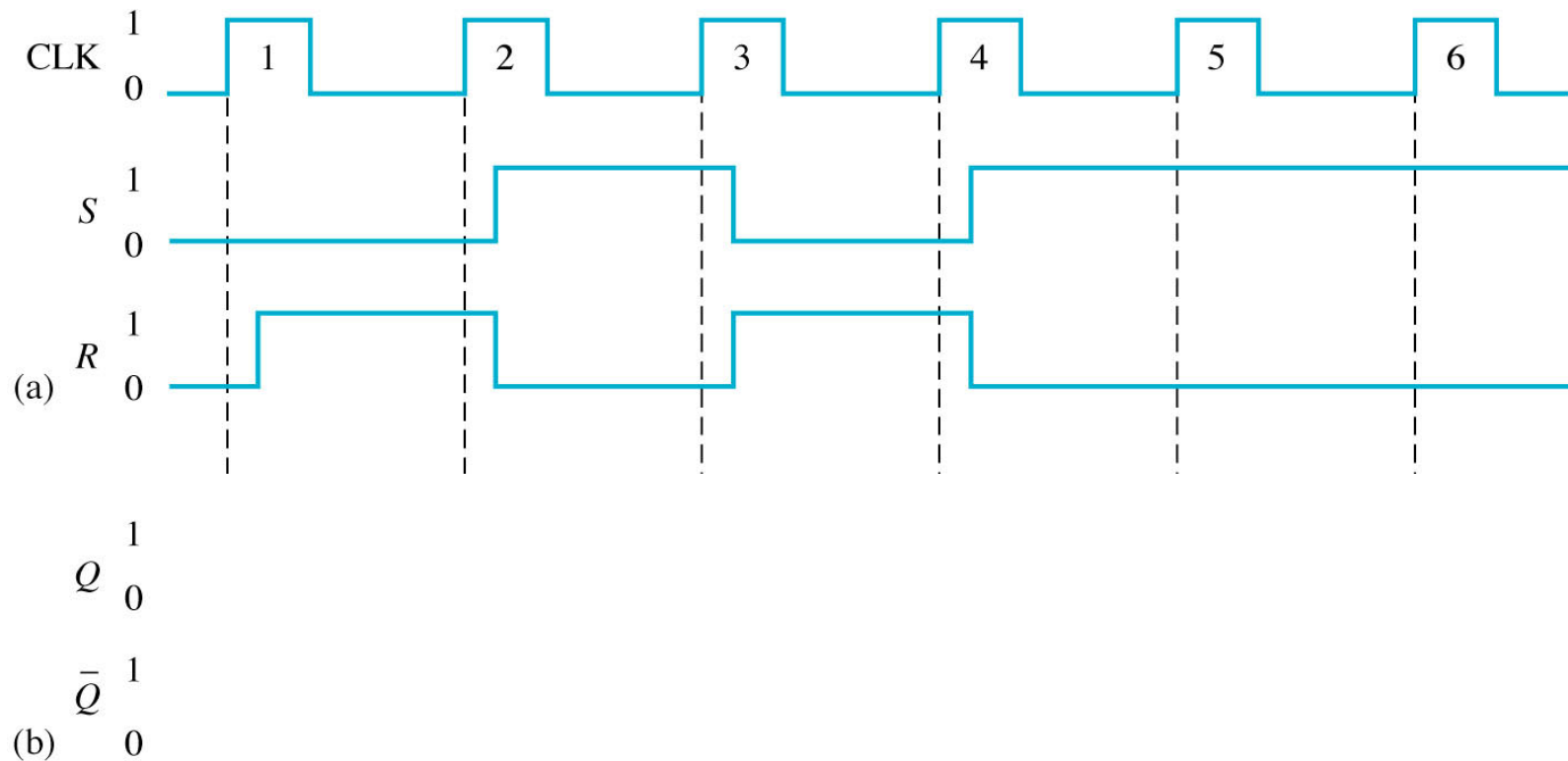**Example:** S-R Flip-Flop.

Find the waveform for  $Q$  and  $\bar{Q}$ .

Assume that the positive edge-triggered flip-flop is initially RESET.




S-R Flip-Flop.


Find the waveform for Q and Q bar.


Assume that the flip-flop is initially RESET.

**Solution:**

 

Logic symbol

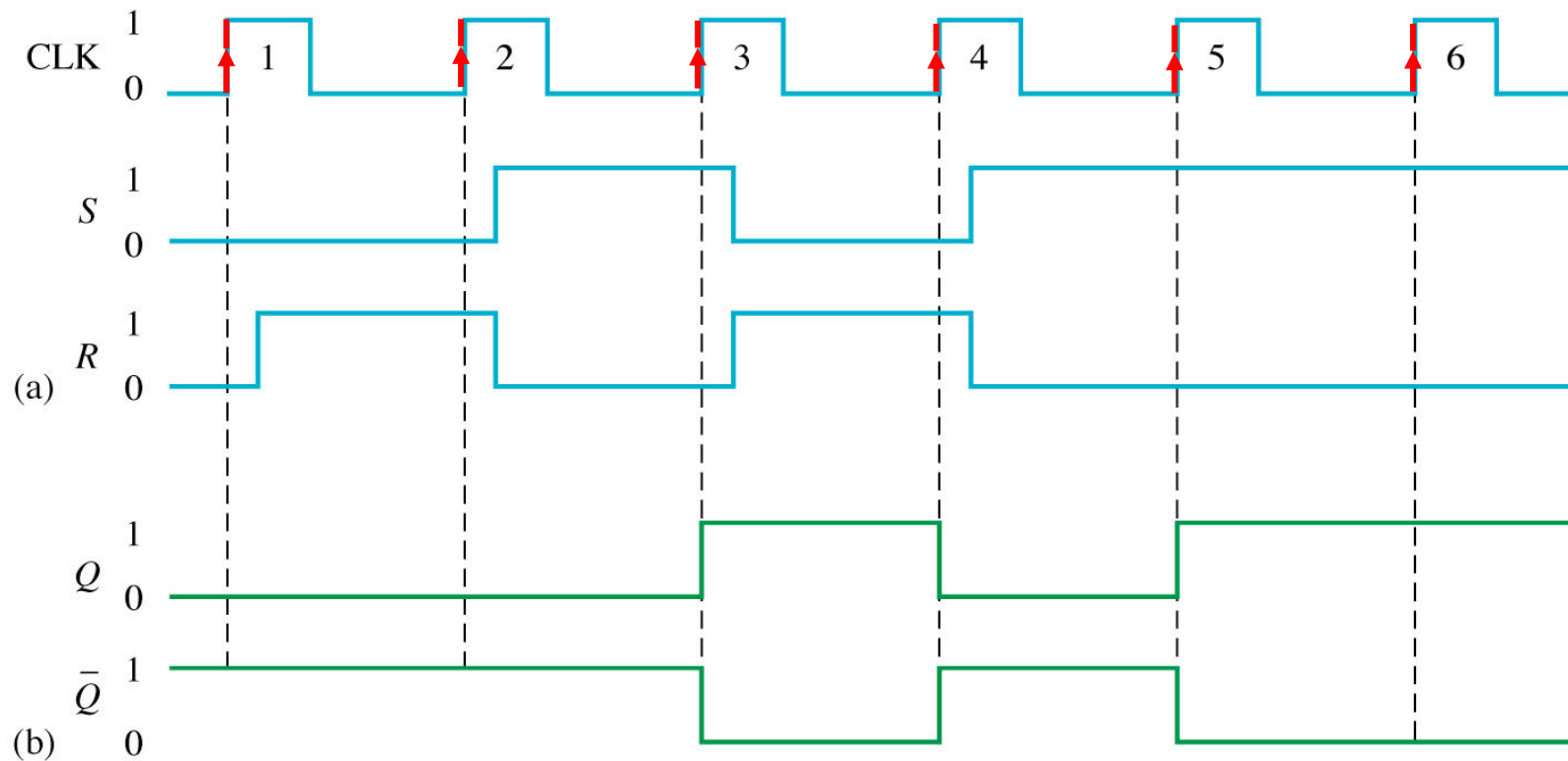

 


Once Q is determined,  $\bar{Q}$  is easily found since it is simply the complement of Q.

Clock Pulse	S	R	Q
1	0	0	Does not change
2	0	1	LOW (RESET)
3	1	0	HIGH (SET)
4	0	1	LOW (RESET)
5	1	0	HIGH (SET)
6	1	0	Stay HIGH
 
### Exercise 7.3:

Given the inputs  $S$  and  $R$  for Gated S-R Latch with the output  $Q_1$ , and for flip-flop with output  $Q_2$ . Find the waveforms for  $Q_1$  and  $Q_2$ . Assume that both outputs are initially LOW and the flip-flop activated at positive edge-triggered.






### Solution 7.3:

Gated S-R Latch with the output  $Q_1$


-> waveforms for  $Q_1$  :

 

### Solution 7.3:


Flip-flop with output  $Q_2$  and activated at **positive edge-triggered**

-> waveforms for  $Q_2$ .

 

 
### Solution 7.3:

Combined waveforms for  $Q_1$  and  $Q_2$  :


 
### Self-Test:


If a S-R Latch is used with output  $Q_3$ , find the waveforms for  $Q_3$ . Is the waveforms  $Q_3$  similar to the waveform  $Q_1$  in Exercise 7.3. Justify your answer. Assume that the outputs are initially LOW.



$Q_3$

 
### Self-Test:

S-R Latch is used with output  $Q_3$ , ... the waveforms for  $Q_3$ .


 
### Self-Test:


Is the waveforms  $Q_3$  similar to the waveform  $Q_1$  in Exercise 7.3 ? Justify your answer.




## (ii) J-K Flip-Flop

- The JK FF is versatile and is a widely used type of FF.
- The difference between J-K and S-R:

J-K has **no invalid state** as S-R.

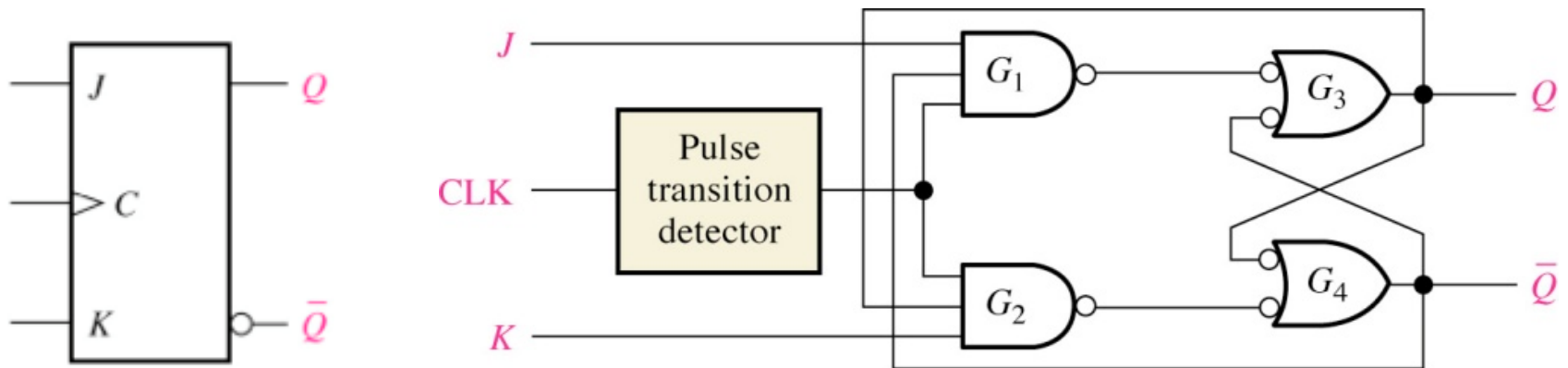

Logic Symbol

 

Logic symbol

J	K	CLK	Output		Comments
			Q	$\bar{Q}$	
0	0	$\uparrow/\downarrow$	$Q_0$	$\bar{Q}_0$	No Change
0	1	$\uparrow/\downarrow$	0	1	RESET
1	0	$\uparrow/\downarrow$	1	0	SET
1	1	$\uparrow/\downarrow$	$\bar{Q}_0$	$Q_0$	Toggle

## TRUTH TABLE



$\uparrow$  = clock transition LOW to HIGH

$Q_0$  = output level prior to clock transition



**Example:** J-K Flip-Flop.  
Find the waveform for Q.  
Assume that Q is initially LOW.

Positive  
or  
negative  
triggered?

  



Logic symbol

**Solution:**

J	K	CLK	Output		Comments
			Q	$\bar{Q}$	
0	0	$\uparrow/\downarrow$	$Q_0$	$\bar{Q}_0$	No Change
0	1	$\uparrow/\downarrow$	0	1	RESET
1	0	$\uparrow/\downarrow$	1	0	SET
1	1	$\uparrow/\downarrow$	$\bar{Q}_0$	$Q_0$	Toggle

Positive triggered


When the output toggled?

 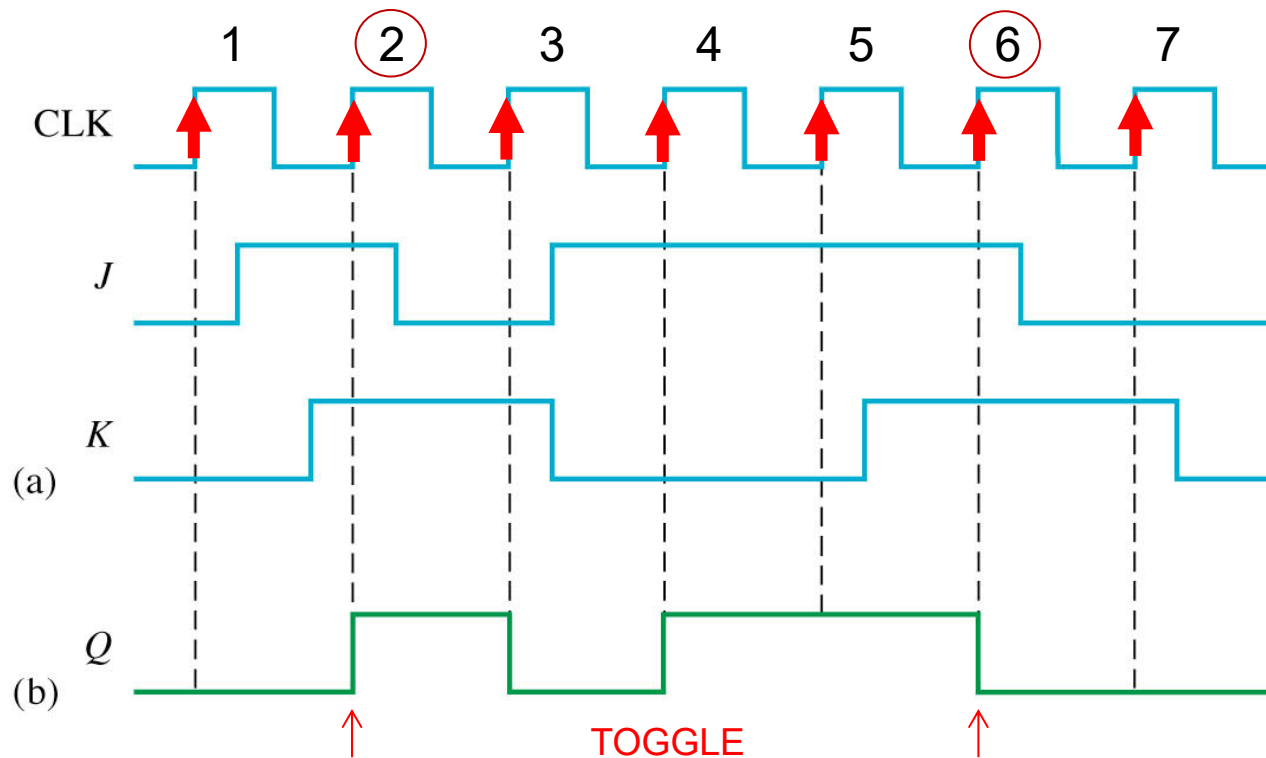

Logic symbol

**Example:** J-K Flip-Flop.  
Find the waveform for Q.  
Assume that Q is initially LOW.



Positive  
or  
negative  
triggered?

 

Solution:

J	K	CLK	Output		Comments
			Q	$\bar{Q}$	
0	0	$\uparrow/\downarrow$	$Q_0$	$\bar{Q}_0$	No Change
0	1	$\uparrow/\downarrow$	0	1	RESET
1	0	$\uparrow/\downarrow$	1	0	SET
1	1	$\uparrow/\downarrow$	$\bar{Q}_0$	$Q_0$	Toggle



negative triggered

  
  
### (iii) D Flip-Flop

D → Data or Delay


- D FF is useful when a single data bit (1 or 0) is to be stored.
- The addition of an **inverter** to an S-R FF creates basic D FF where a **positive edge-triggered** type is shown below:



Logic symbol


## TRUTH TABLE

INPUTS		OUTPUTS		COMMENTS
D	CLK	Q	$\bar{Q}$	
1	↑	1	0	SET (store a 1)
0	↑	0	1	RESET (store 0)

 

Logic symbol



(for positive edge-triggered)

 

Remember, Q follows D at the active triggering clock edge.
  
## (iv) T Flip-Flop


- Also called as **toggle** flip-flop.
- Frequently used in building **counters**.



Logic Symbol


## TRUTH TABLE

T	CLK ↑/↓	Output		Comments
		Q	Q <sub>next</sub>	
0	↑/↓	0	0	HOLD
0	↑/↓	1	1	HOLD
1	↑/↓	0	1	TOGGLE
1	↑/↓	1	0	TOGGLE

 

Logic symbol

 
Timing  
Diagram for  
T Flip-Flop  
(Negative-  
Edge  
Triggered)






Try :

 Consider a positive-edge trigger for a T-FF. Draw the waveforms for Q. Assume that the output is initially LOW.




Logic symbol

 

**Exercise 7.4:**

Given the inputs  $S$  and  $R$  for flip-flop with the inputs always complement to each other and activated at negative edge-triggered.


 
- (i) Draw the logic symbol for the flip-flop.
- (ii) Find the waveforms  $Q$ . Assume that the output is initially LOW.





  
## JK Flip Flop with Asynchronous Input

- The J and K inputs are called **synchronous inputs** since they only influence the state of the flip flop when the **clock** input is present.
- Synchronous → J and K inputs transferred on the triggering edge of the clock



 
## JK Flip Flop with Asynchronous Input

- This flip flop can also have **other inputs** called **Preset** and **Clear** that can be used for **setting** the flip flop to **1** or **resetting** it to **0**.
- Asynchronous → These inputs can **change the state** of the flip flop regardless of the clock signal.
  - Preset ( $\overline{\text{PRE}}$ ) or Direct SET
  - Clear ( $\overline{\text{CLR}}$ ) or Direct RESET



## TRUTH TABLE

 

$\overline{PRE}$	$\overline{CLR}$	FF	MODE
0	1	SET	Asynchronous
1	0	RESET	Asynchronous
1	1	JK	Synchronous
0	0	-	-

**FF Response:**

$Q = 1$

$Q = 0$

*FF Clock Working*

*Not Used*

- Flip-flop input priority:

Priority	FF Input
Highest	$\overline{PRE}, \overline{CLR}$ (Asynchronous input)
Medium	Clock
Lowest	J-K, S-R, D, T (Synchronous input)


- Flip-flop asynchronous input has the highest priority.
  - Which means that if the asynchronous input active, the output will immediately change regardless the value of synchronous input or clock.

$\overline{PRE}$	$\overline{CLR}$	FF
0	1	SET
1	0	RESET
1	1	JK


(Module: page 231)

 **Note:**


When  $J = K = 1$ ,  
it works as **T flip-flop**



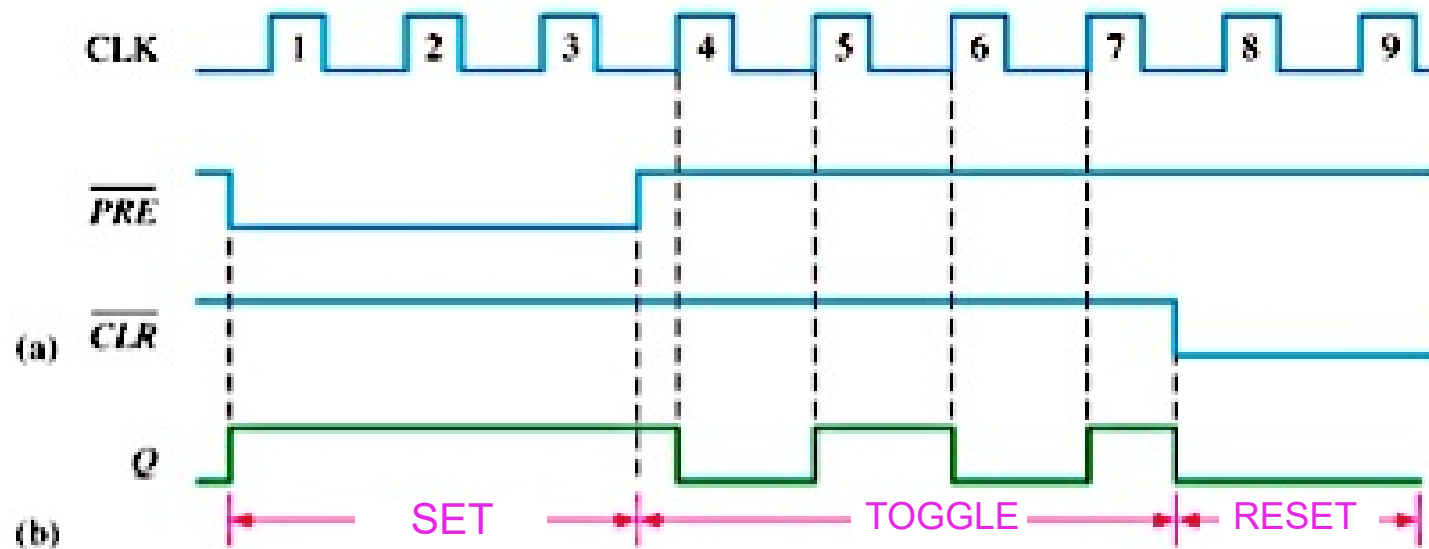**Example:** J-K Flip-Flop with both inputs are HIGH.  
Find the waveform for Q.  
Assume that Q is initially LOW.



$\overline{PRE}$	$\overline{CLR}$	$FF$	MODE
0	1	SET	Asynchronous
1	0	RESET	Asynchronous
1	1	JK	Synchronous

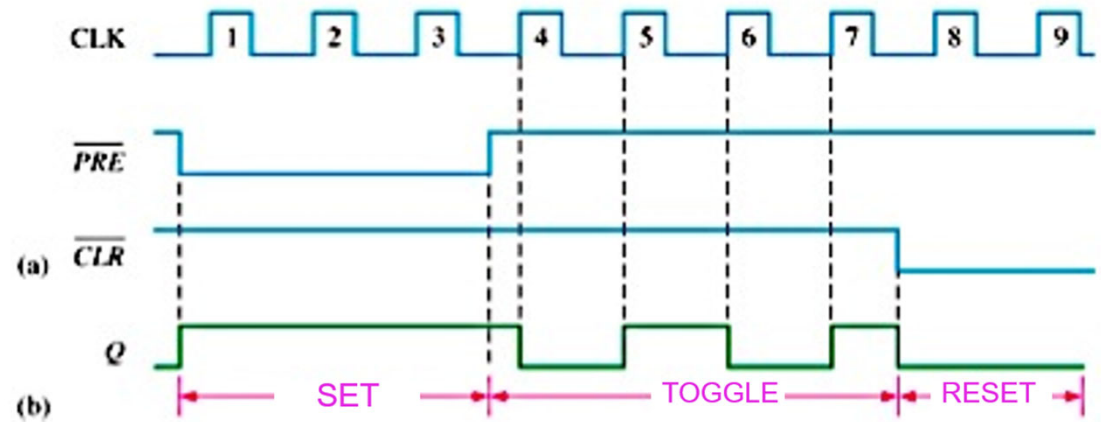


<i>clk pulse</i>	$\overline{PRE}$	$\overline{CLR}$	$J$	$K$	$Q$ $FF$	Comment
1,2,3	0	1	1	1	SET	JK inputs - dont care
4,5,6,7	1	1	1	1	Toggle	Synchronous mode.
8,9	1	0	1	1	RESET	JK inputs - dont care

**Exercise 7.5:**

Find the waveform for Q.

Assume that asynchronous J-K FF is used with both inputs are HIGH, and Q is initially LOW.

 




**Exercise 7.6:**

Find the waveform for Q for asynchronous J-K FF.

Assume that Q is initially HIGH.

 

**Exercise 7.7:** Complete the table in sequence.

Assume a J-K flip-flop is used with  $\overline{PRE}$  and  $\overline{CLR}$  inputs, and output Q.

$\overline{PRE}$	$\overline{CLR}$	J	K	Q	Mode	Comment
1	1	1	0			
1	1	1	1			
0	1	0	1			
1	1	0	0			
1	0	1	0			
0	1	1	1			
1	1	0	0			
1	1	1	1			

Mode: (Asynchronous / Synchronous)

Comment: (SET / RESET / HOLD / TOGGLED / PRESET / CLEAR / INVALID)



# Summary

## Latch & Flip-Flop

	Latch	Gated Latch	Flip-Flop
Output Characteristics	<p>Output / next state depends to:</p> <ul style="list-style-type: none"><li>• current inputs &amp;</li><li>• previous outputs / state</li></ul>	<p>Output / next state depends to</p> <ul style="list-style-type: none"><li>• enable gate input</li><li>• current inputs</li><li>• previous outputs / state</li></ul>	<p>Output / next state depends to:</p> <ul style="list-style-type: none"><li>• edge-triggered clock</li><li>• current inputs</li><li>• previous outputs / state</li></ul>

# S-R Latch/FF

## Block Diagram

### Basic Operation Truth-table


S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	-	-

For:


- En = 1 (Gated Latch)

-  &  FF

### Latch

 


### Gated Latch

 

S	R	En	Q	Q'
0	0	1	Q	Q'
0	1	1	0	1
1	0	1	1	0
1	1	1	-	-
X	X	0	Q	Q'

### Flip-Flop

 

# D Latch/FF


## Block Diagram

### Basic Operation Truth-table


D	Q	Q'
0	0	1
1	1	0

For:


- En = 1 (Gated Latch)

-  &  FF

### Latch


 



### Gated Latch

 

D	En	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q	Q'

### Flip-Flop

  

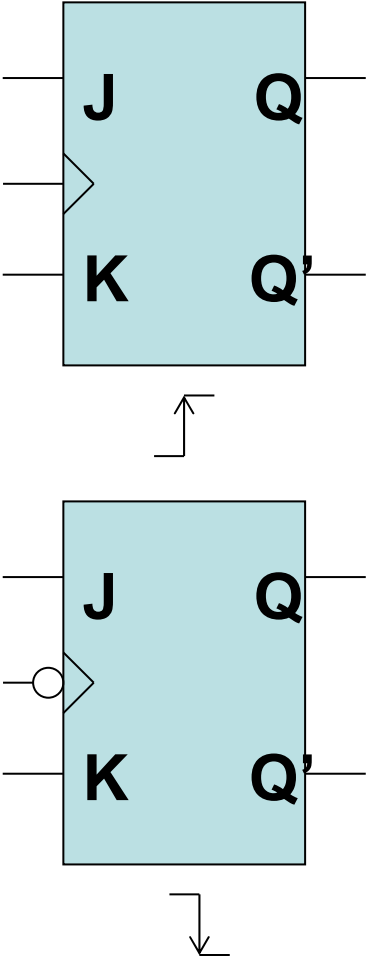J-K FF	Block Diagram																						
Basic Operation Truth-table	Latch	Gated Latch	Flip-Flop																				
<table border="1"> <thead> <tr> <th>J</th><th>K</th><th>Q</th><th>Q'</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>Q</td><td>Q'</td></tr> <tr> <td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>Q'</td><td>Q</td></tr> </tbody> </table>	J	K	Q	Q'	0	0	Q	Q'	0	1	0	1	1	0	1	0	1	1	Q'	Q	Nil	Nil	
J	K	Q	Q'																				
0	0	Q	Q'																				
0	1	0	1																				
1	0	1	0																				
1	1	Q'	Q																				

## Asyn. J-K FF

## Block Diagram

### Basic Operation Truth-table

Latch

Gated Latch

Flip-Flop

$\overline{PRE}$	$\overline{CLR}$	FF
0	1	SET
1	0	RESET
1	1	JK

J	K	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Q'	Q

Nil

Nil

