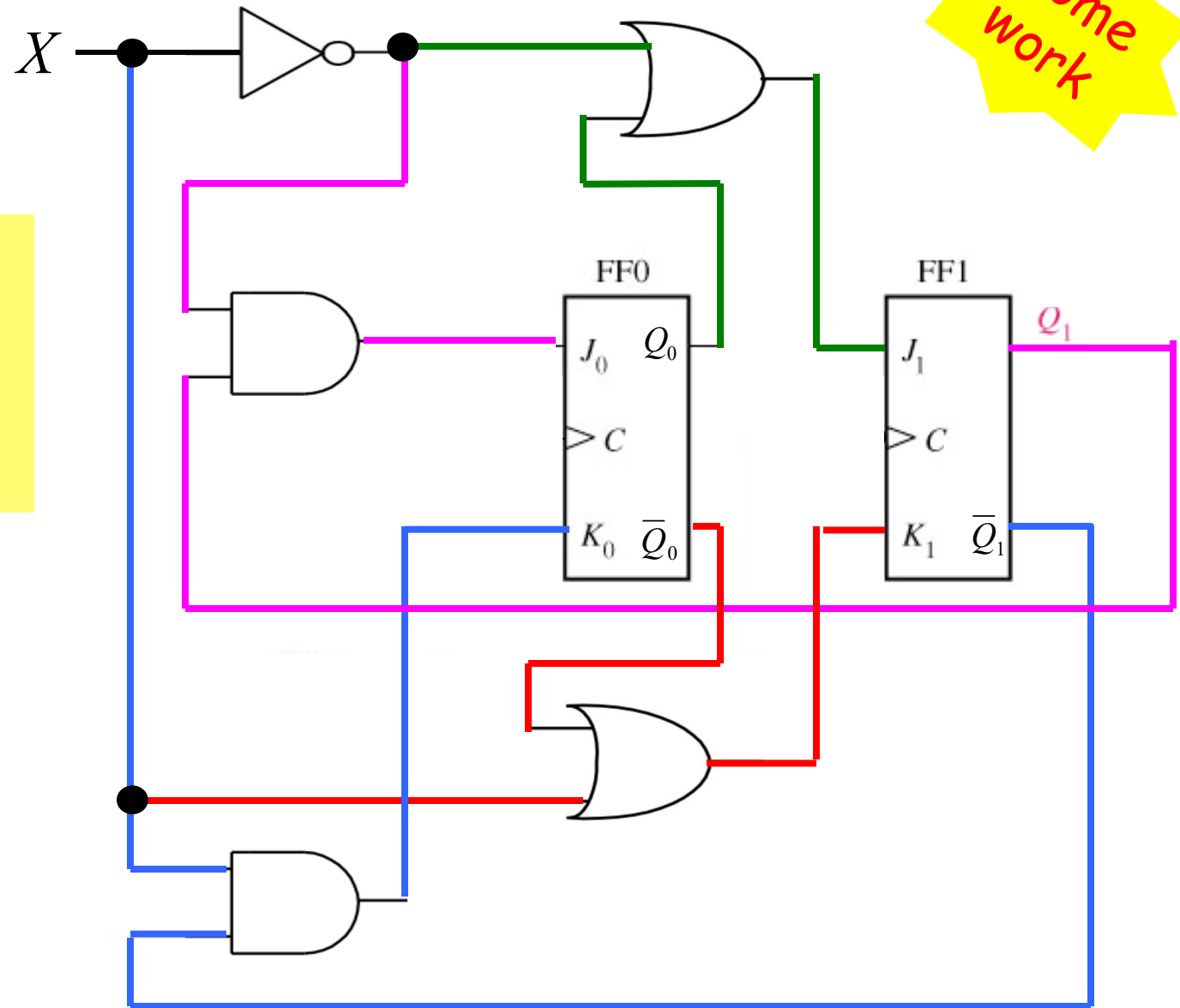


Home  
work

**Exercise 8b.23:**


Derive the state  
table and state  
diagram for the  
sequential circuit  
below.




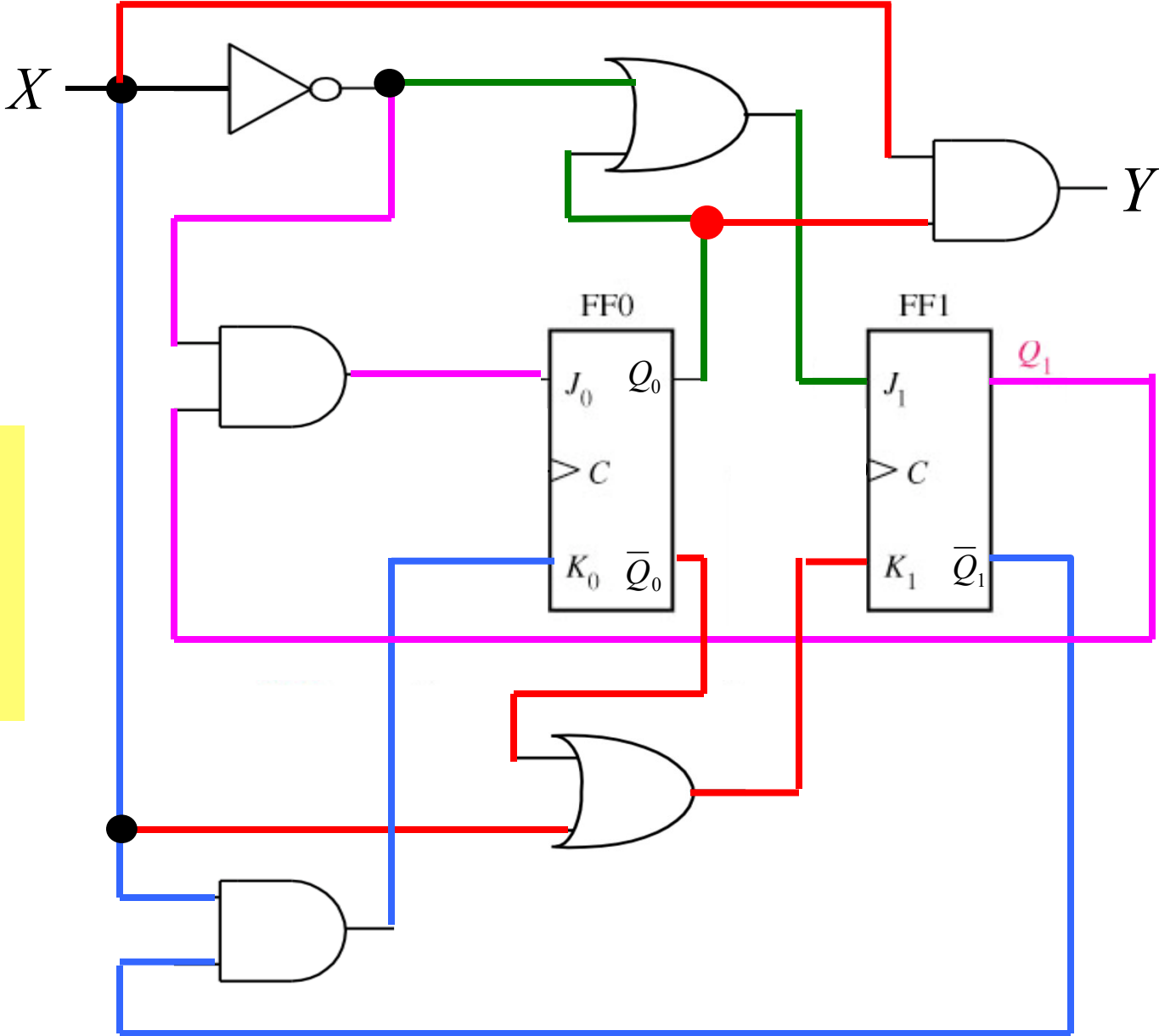
## Exercise 8b.24:


Derive the state table and state diagram for the sequential circuit below.




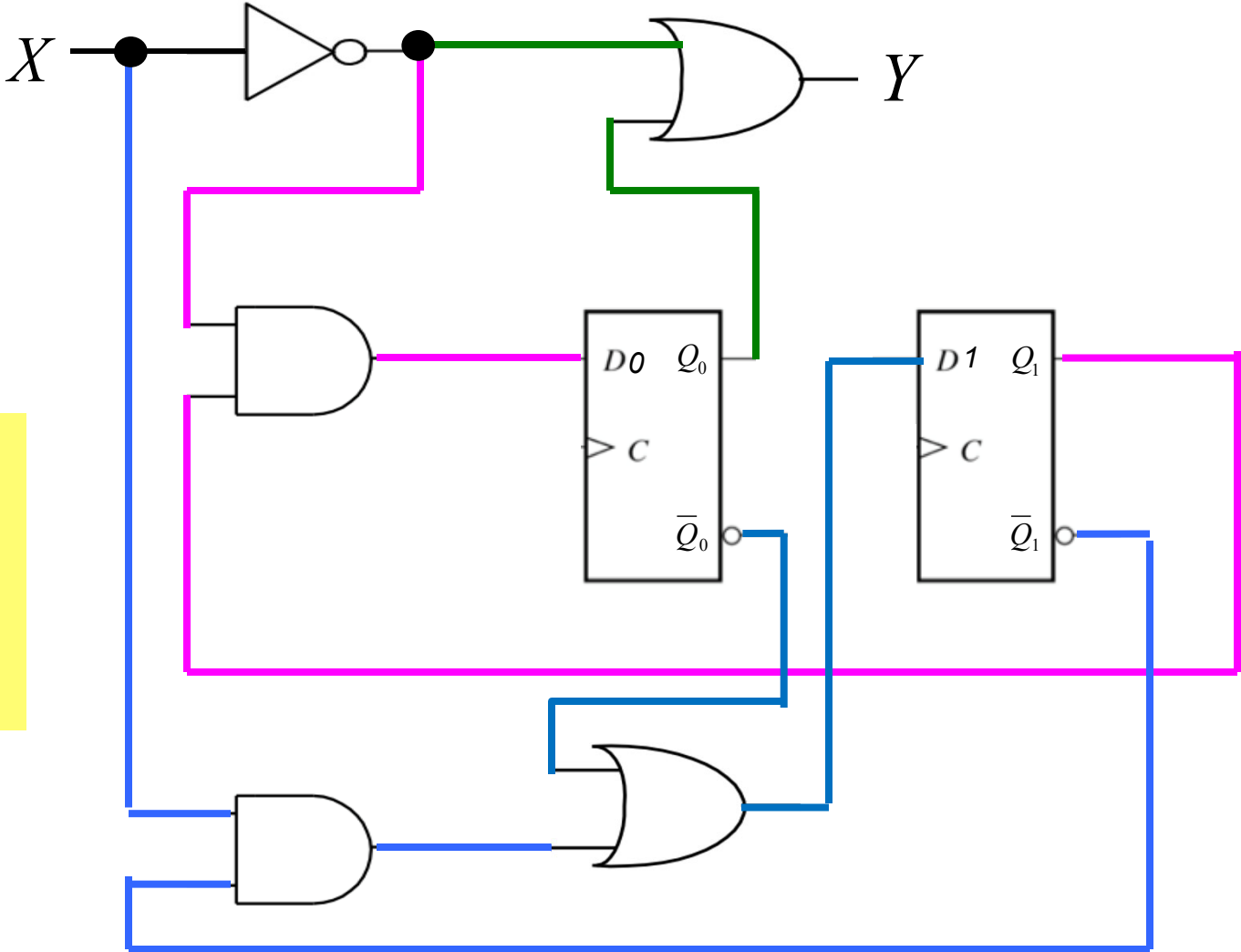
## Exercise 8b.25:

Derive the state table and state diagram for the sequential circuit below.





### Exercise 8b.27:

Derive the state table and state diagram for the sequential circuit below.

